

# CS & IT

NOT GATE , AND ,  
OR GATE



Logic gate

Lecture No. 1



By- CHANDAN SIR



Sat.  
Sun.

{ 4:00 PM - 6:00 PM  
6:30 PM - 8:30 PM }

TOPICS TO BE  
COVERED

01 Syllabus

02 Weightage

03 Reference Books

04 NOT GATE

05 AND GATE

OR GATE



## Digital Logic

✓  
*Designing*  
Boolean algebra Combinational and sequential circuits. Minimization.  
Number representations and computer arithmetic (fixed and floating point).

*B.A.*


*K-Map*

## DIGITAL LOGIC

No. of Questions	2 to 4
Marks	4 to 6 ✓
Frequently Asked Topics	Boolean algebra. Combinational and sequential circuits. Minimization. Number representations



# Reference Books

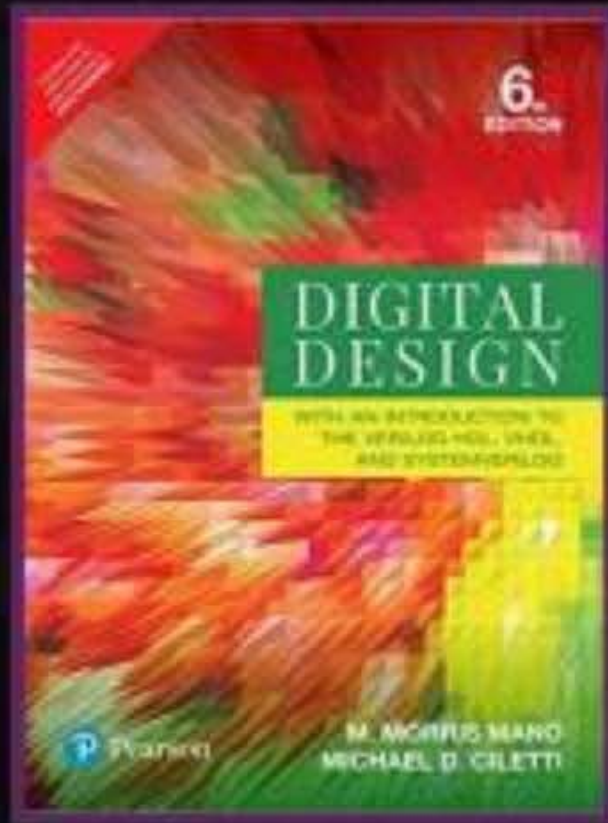

**Book Name:** Digital Design  
**Author:** M. Morris Mano & Michael D. Ciletti  
**Publisher:** Pearson Publishers



**Book Name:** Digital fundamental  
**Author:** Thomas L. Floyd  
**Publisher:** Pearson Publishers




## Guidelines to Attend Live Class



- ✓ Attend the class with positive attitude.
- ✓ Punctuality is necessary. ✓
- ✓ Follow the day-wise study plan. ✓
- ✓ Attempt DPP daily as per the schedule.
- ✓ Hold chat while attending the class. We will allow you to ask and put your questions in the comment box.

## CLASS NOTES

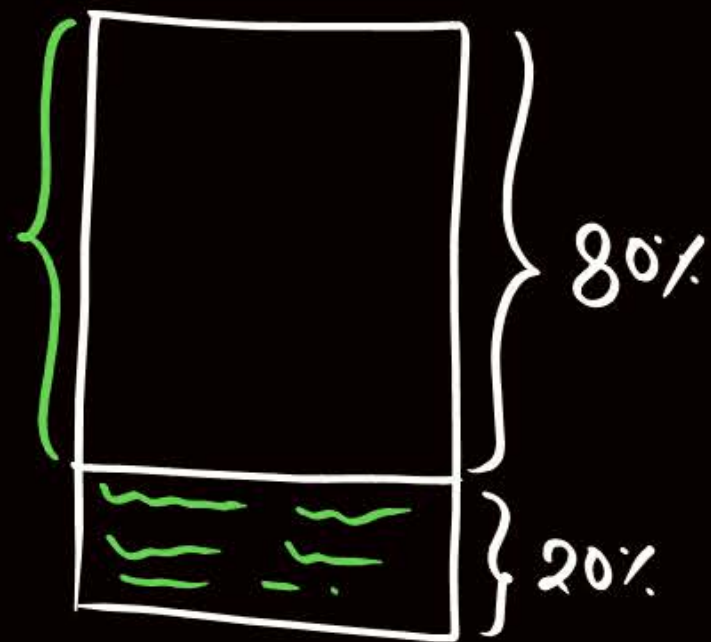

chapter-1

20 pages

2 pages


chupke

~~300 pages~~

✓ Short NOTES



GATE-O-PEDIA

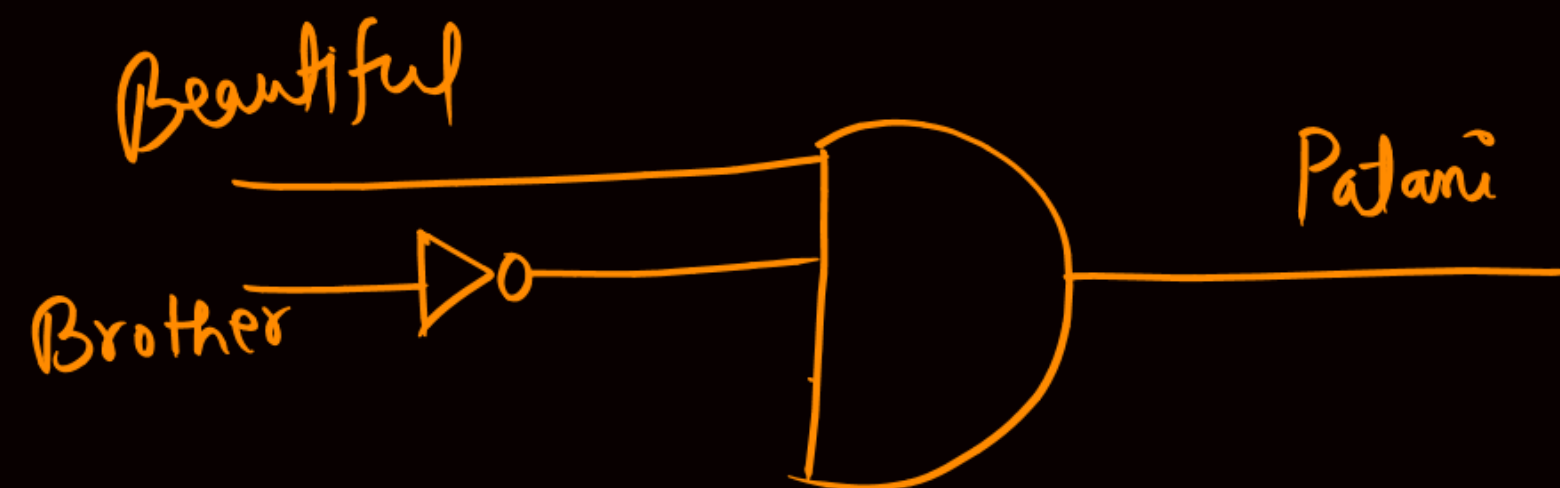



(CS)✓



S.N.	Chapter	TOPIC
1	Logic Gate	NOT, AND, OR, NAND, NOR, X-OR, X-NOR
2	Minimization	Boolean algebra, K-MAP
3	Combinational Circuit	Designing, Comparator, MUX, DE-MUX, Encoder, Decoder, HA, FA, HS, FS, Serial adder, parallel adder, LCA
4	Sequential Circuit	Latches, Flip-Flops, Registers, counters
5	Number System	Base conversion, Magnitude Representation

Questions.

DPP → 150 question

Theory → NOTES.

① Previous Year GATE → 20 years.

Books  $\left\{ \begin{array}{l} \text{unsolved} \checkmark \\ \text{solved} \checkmark \end{array} \right.$

$\left\{ \begin{array}{l} \rightarrow \text{CS} \rightarrow 300 \\ \rightarrow \text{EC} \rightarrow 300 \\ \rightarrow \text{EE} \rightarrow 300 \\ \rightarrow \text{IN} \rightarrow 300 \\ \hline 1200 \end{array} \right\}$

$\left\{ \begin{array}{l} \text{Kanodia} \rightarrow 500 \\ \hline 1700 \end{array} \right\}$



# Flip-Flop

JK Flip-Flop

Jack Kilby

papa of IC

IC

Integrated circuit

1 element → 1958

2 element → 1960

4 element → 1962

8 element → 1964

14 years

Gordon E. Moore

Intel

1962 →

"Moore's Law"

1965

statement

Moore's Law

Nobel prize

+ve Logic

0  $\longrightarrow$  Low Voltage

1  $\longrightarrow$  High voltage.


$\left. \begin{array}{l} 1 \longrightarrow 10V \\ 0 \longrightarrow 2V \end{array} \right\} \text{+ve Logic.}$



# INVERTER & AND GATE

## LOGIC GATE

### 1. NOT GATE [INVERTER, NEGATION]

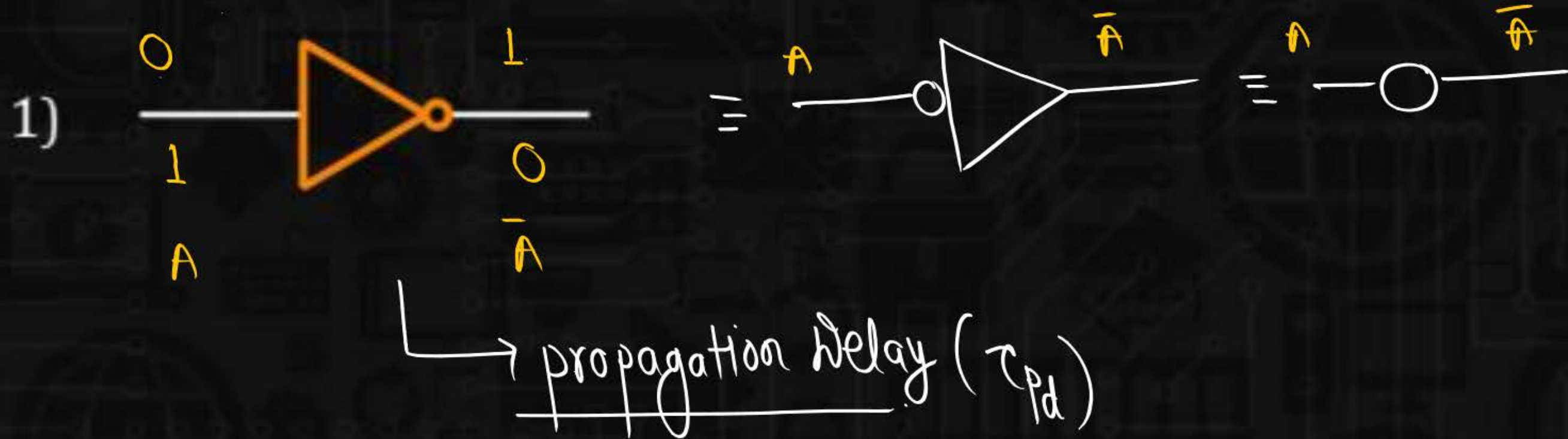


# INVERTER & AND GATE

## LOGIC GATE


### 1. NOT GATE

2)

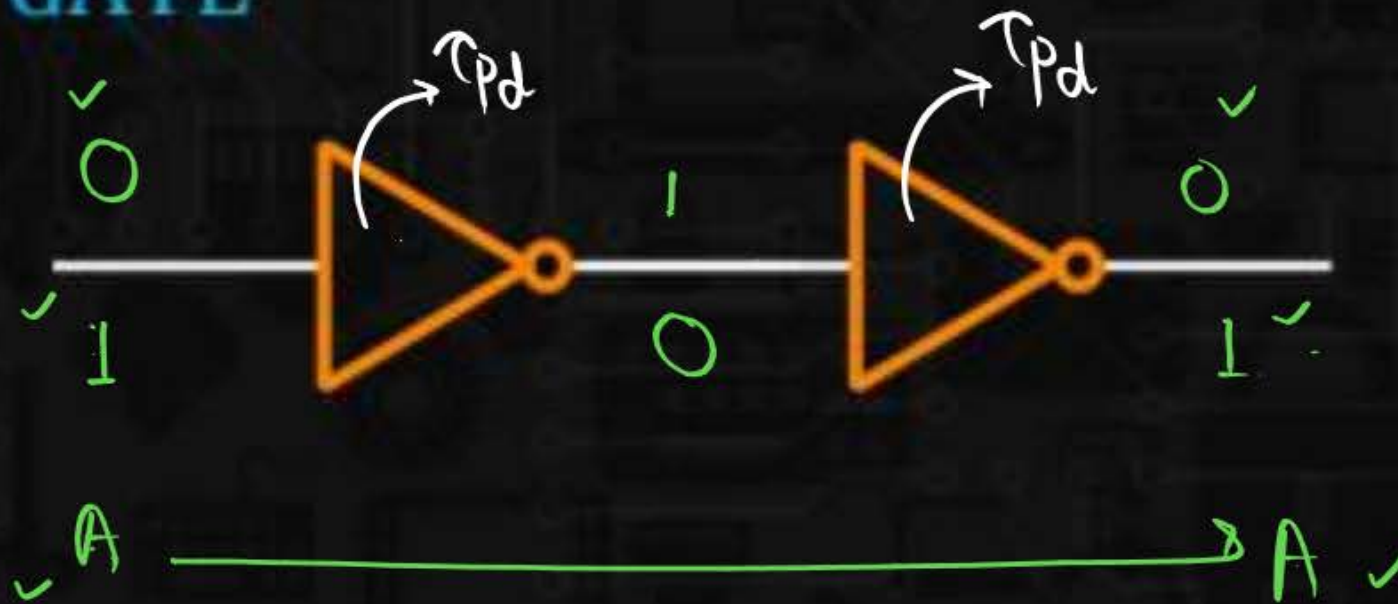

Buffer

used to provide Delay

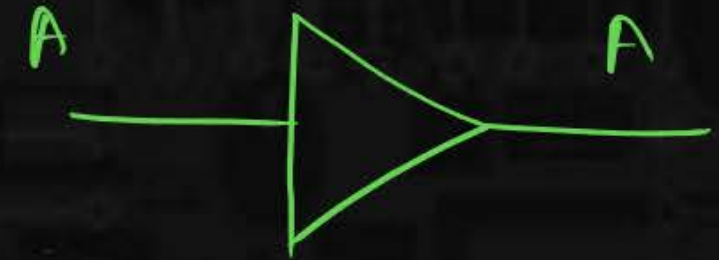




# INVERTER & AND GATE

## LOGIC GATE
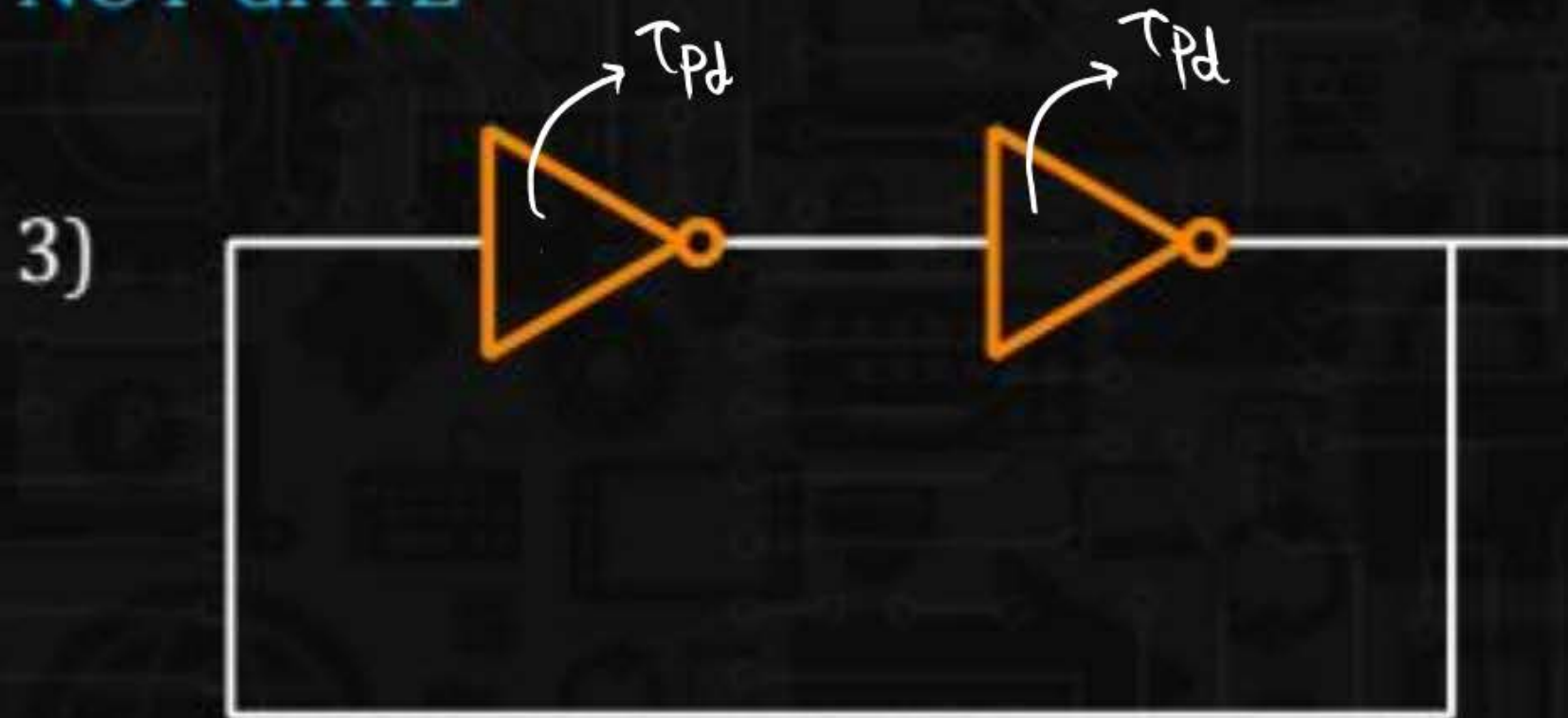
### 1. NOT GATE

When Even no. of NOT GATE.  
in Loop  $\Rightarrow$



$\checkmark \quad 1 \xrightarrow{2\tau_{pd}} 1 \xrightarrow{2\tau_{pd}} 1 \xrightarrow{2\tau_{pd}} \dots$

$\checkmark \quad 0 \xrightarrow{2\tau_{pd}} 0 \xrightarrow{2\tau_{pd}} 0 \xrightarrow{2\tau_{pd}} \dots$

- 1> Basic memory element
- 2> Bistable Multivibrator






# INVERTER & AND GATE

## LOGIC GATE

### 1. NOT GATE


When DO number of NOT GATES in Loop :-

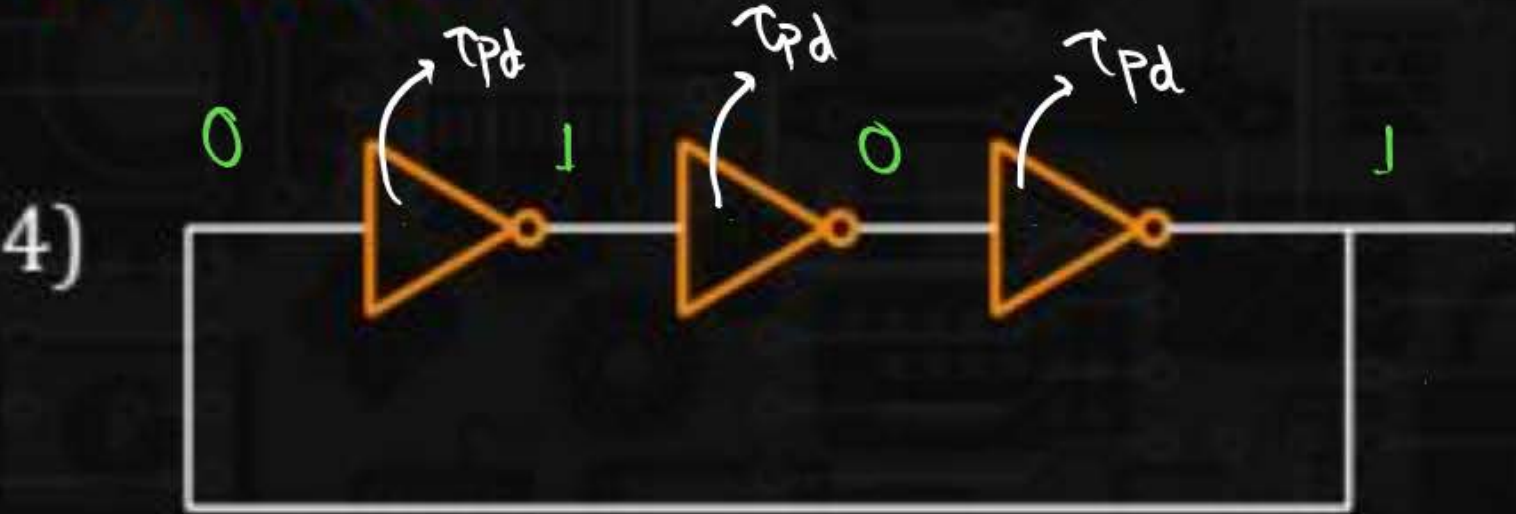

- ① Astable multivibrator
- ② Square wave generator
- ③ clock generator
- ④ Free Running circuit

⑤ Ring oscillator

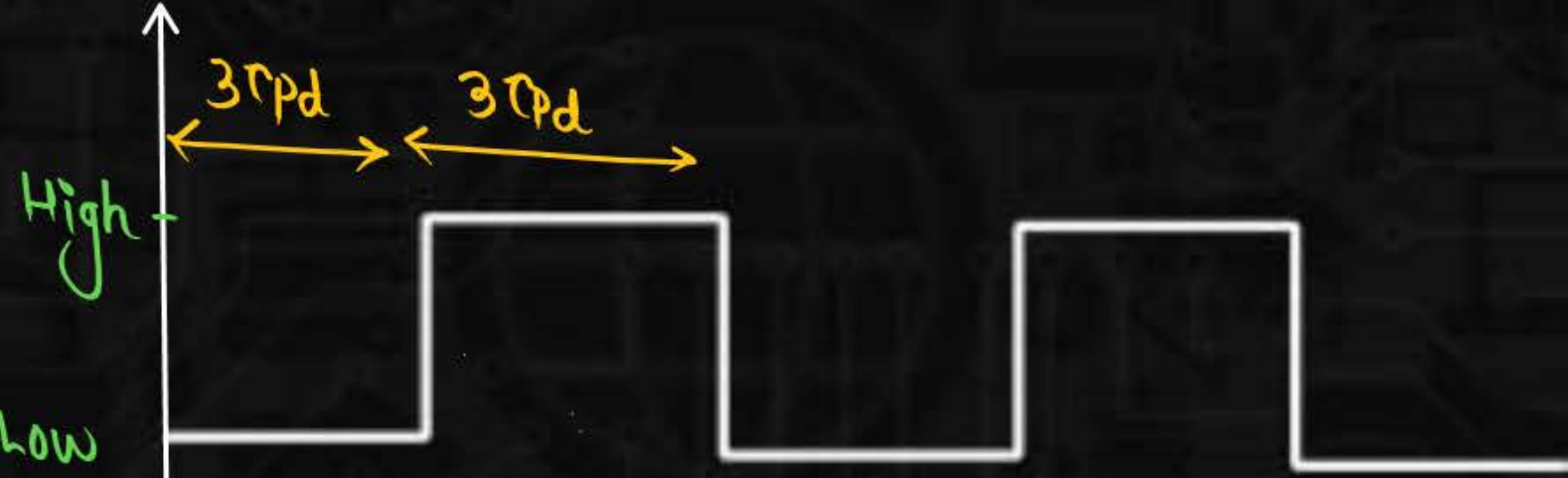$3\tau_{pd}$   $3\tau_{pd}$   $3\tau_{pd}$   $3\tau_{pd}$   
 $0 \rightarrow 1 \rightarrow 0 \rightarrow 1 \rightarrow$



$T = 6\tau_{pd} = 2 \times 3\tau_{pd}$

$T = 2 \times N \times \tau_{pd}$



$$T = 2 \times N \times \tau_{pd}$$

$N \rightarrow$  No. of NOT GATE in Loop

$\tau_{pd} \rightarrow$  Propagation Delay of NOT GATE

★

$$f = \frac{1}{T} = \frac{1}{2N \times \tau_{pd}}$$

**Q.1**


For the circuit given below, all NOT Gates are identical to each other and having propagation delay 10 ps. Find the frequency of generated wave form?

$\rightarrow 10^{-12}$

$$f = \frac{1}{2N \times \tau_{pd}}$$

$$\tau_{pd} = 10 \times 10^{-12} \text{ sec}$$

$$N \rightarrow 5$$

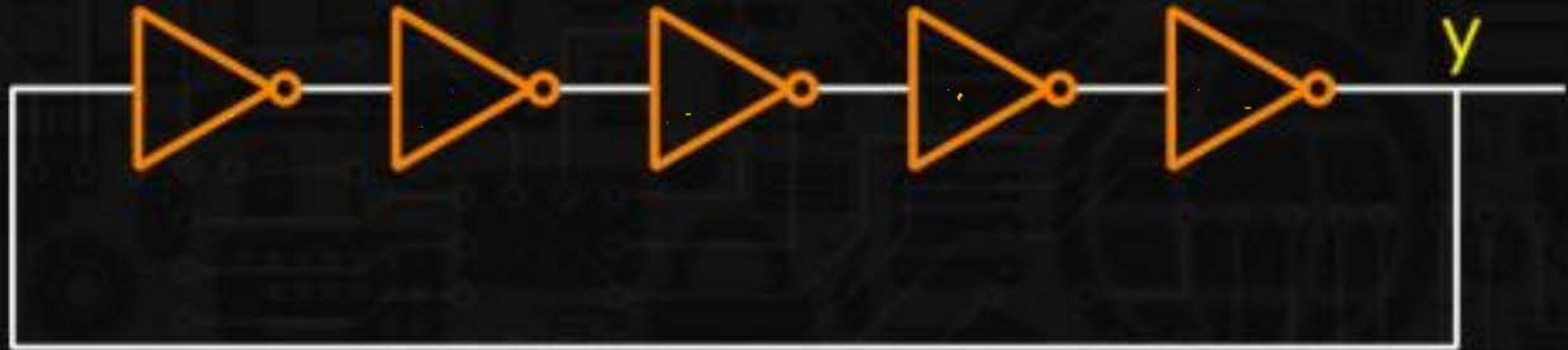

$$f = \frac{1}{2 \times 5 \times 10 \times 10^{-12}} \text{ Hz}$$

$$f = \frac{10^{12}}{10 \times 10} \text{ Hz} = \frac{1000 \times 10^9}{10 \times 10} \text{ Hz}$$


$$= 10 \times 10^9 \text{ Hz}$$

$f = 10 \text{ GHz}$



Q.2


Circuit given below are called.

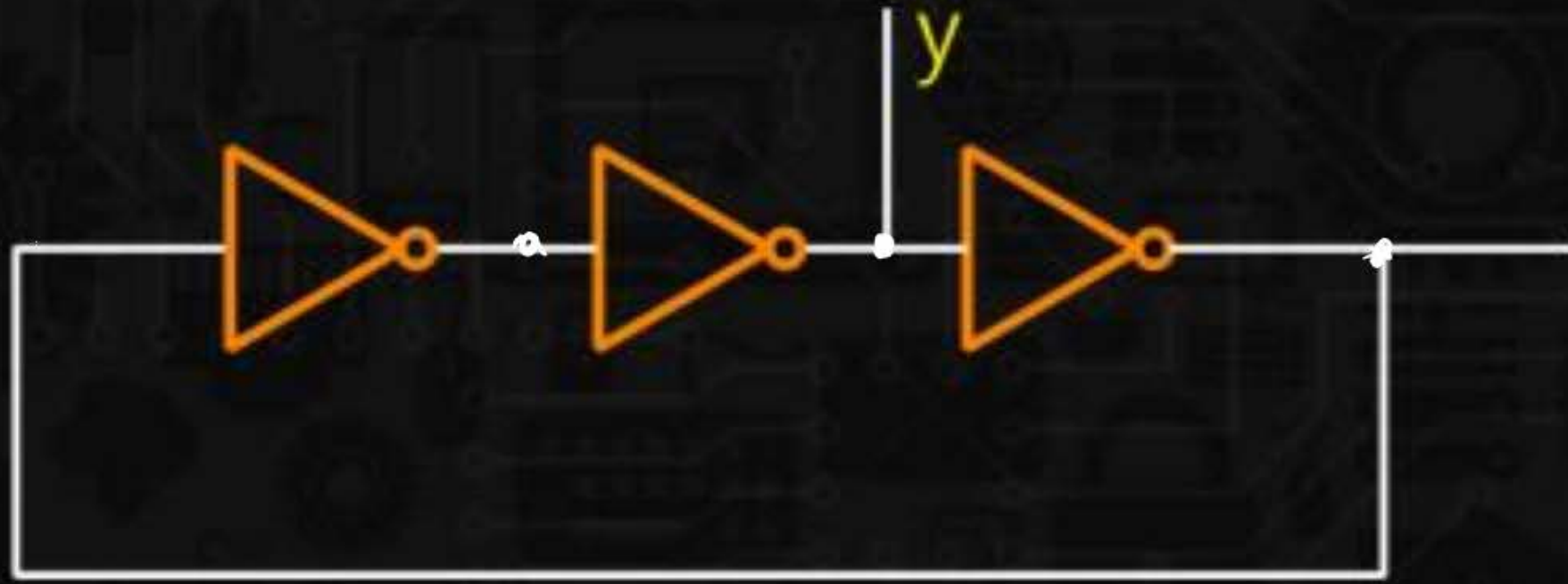

- (A) Astable multivibrator
- (B) Bistable multivibrator

**Q.3** Sketch the waveform of  $y$ ?

HW

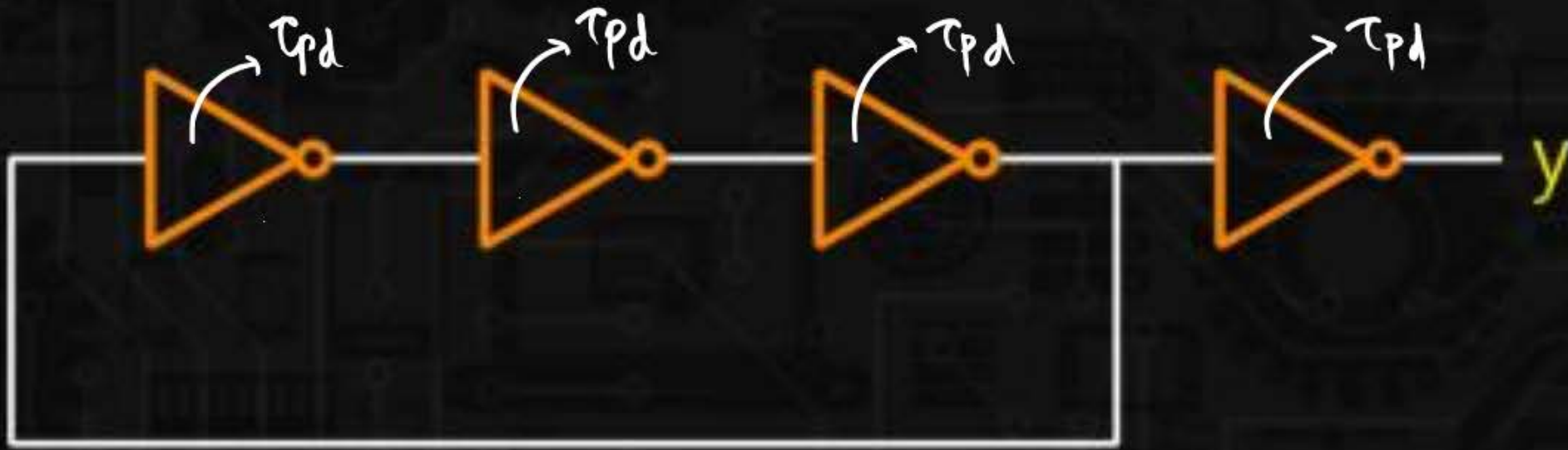



**Q.4**

For the circuit given below x & y condition will be—

HW

A.

x stable y toggle

B.

x toggle y stable

C.

x & y both toggle

D.

x & y both stable

