

CS & IT ENGINEERING

DIGITAL LOGIC

Sequential circuit

Lecture No. 3




By- CHANDAN SIR


TOPICS TO BE COVERED

01 FFs

02 Practice

03 Discussion

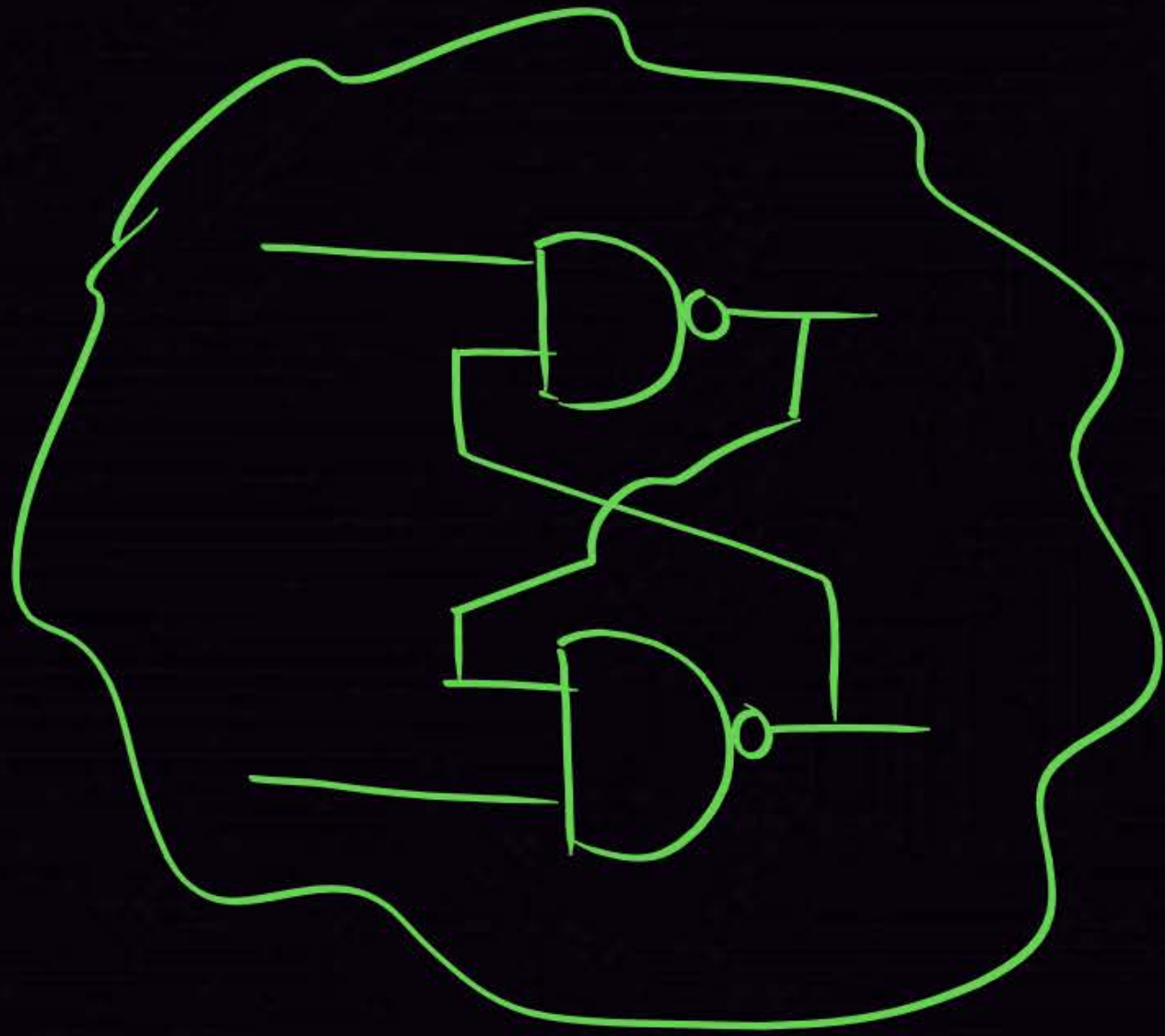

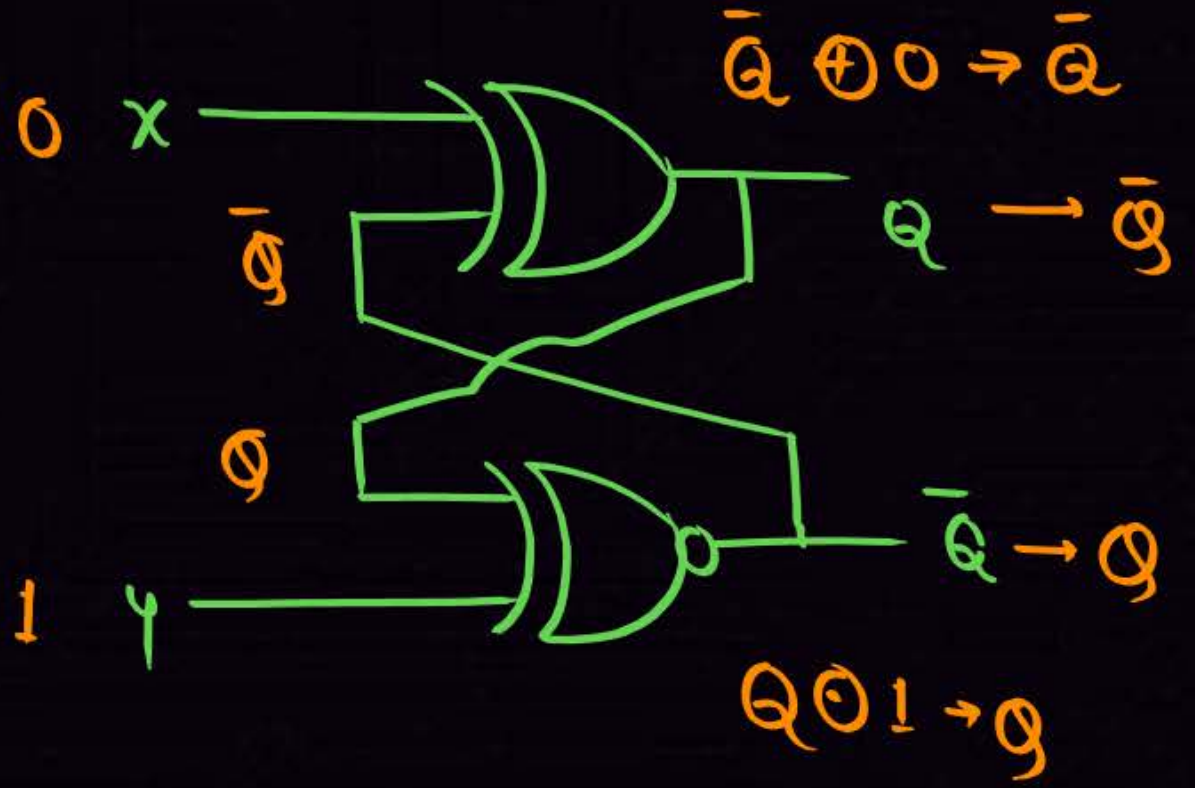

X	Y	Q	\bar{Q}
0	0	\bar{Q}	\bar{Q}
0	1	\bar{Q}	Q
1	0	Q	\bar{Q}
1	1	Q	Q

Invalid condition.
 Toggle
 HOLD / MEMOR / Previous state
 Invalid forbidden don't care.



<u>X-OR</u>	<u>X-NOR</u>	
$Q + Q = 0$	$Q \odot Q = 1$	
$Q + 0 = Q$	$Q \odot 1 = Q$	
$\bar{Q} + 0 = \bar{Q}$	$\bar{Q} \odot 1 = \bar{Q}$	
$Q + \bar{Q} = 1$	$Q \odot \bar{Q} = 0$	$\bar{Q} \odot 0 = Q$
$Q + 1 = \bar{Q}$	$Q \odot 0 = \bar{Q}$	
$\bar{Q} + 1 = Q$		

Level sensitive.

Edge sensitive.

Latch → Control (clock)

Flip-Flop ✓✓

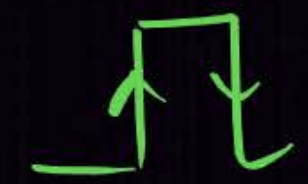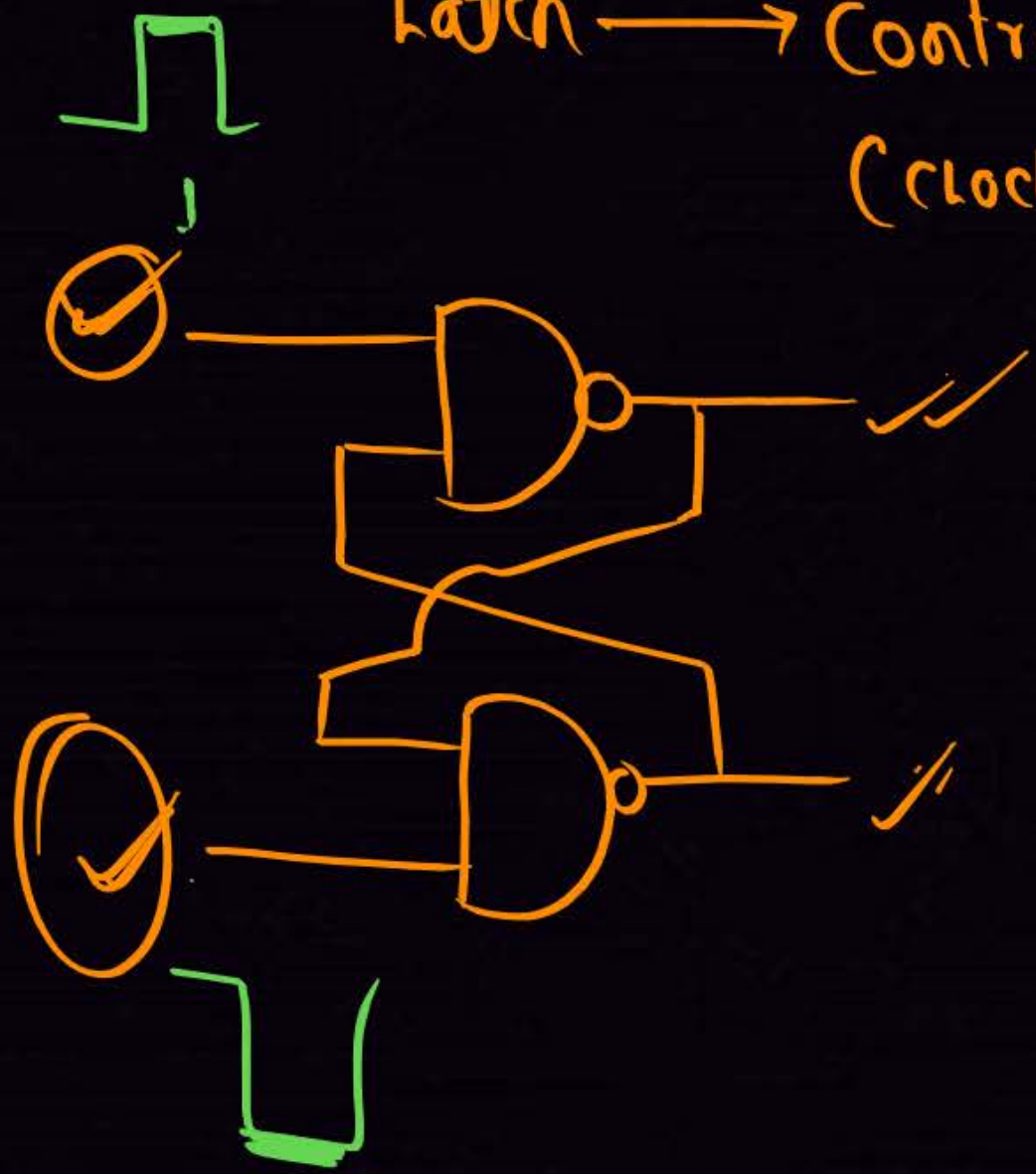

Triggering


Level triggered

Edge triggered


+ve Level








-ve Level

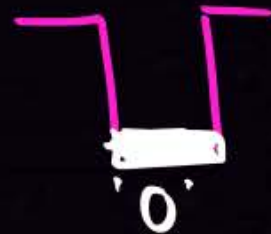


+ve edge

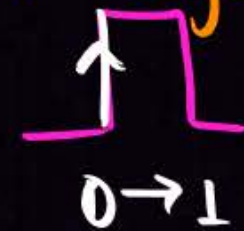




-ve edge

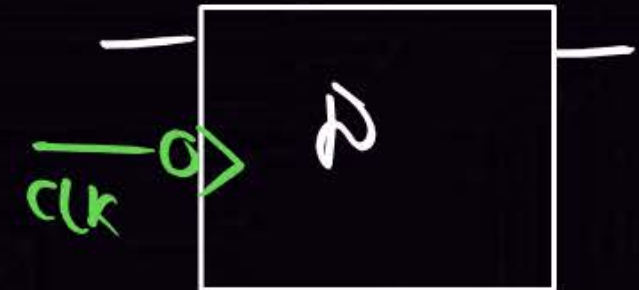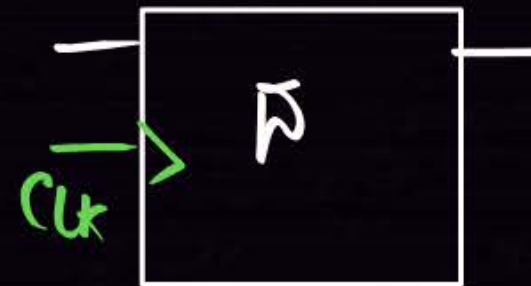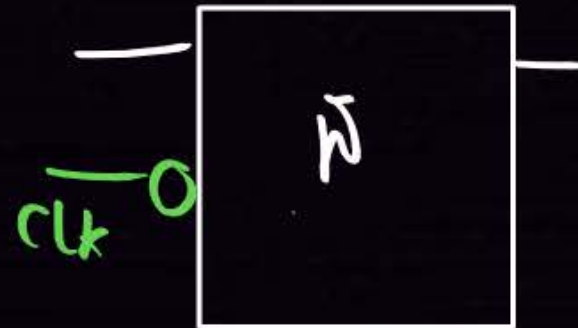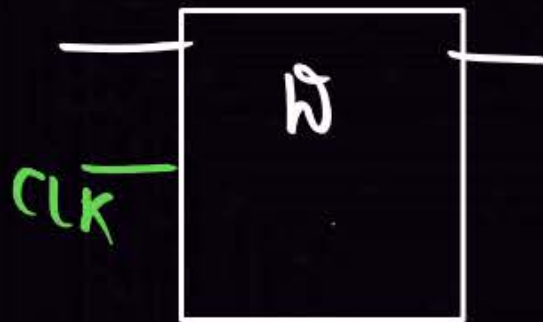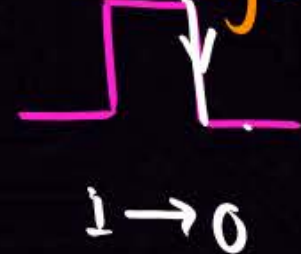


S R - Flip. Flop

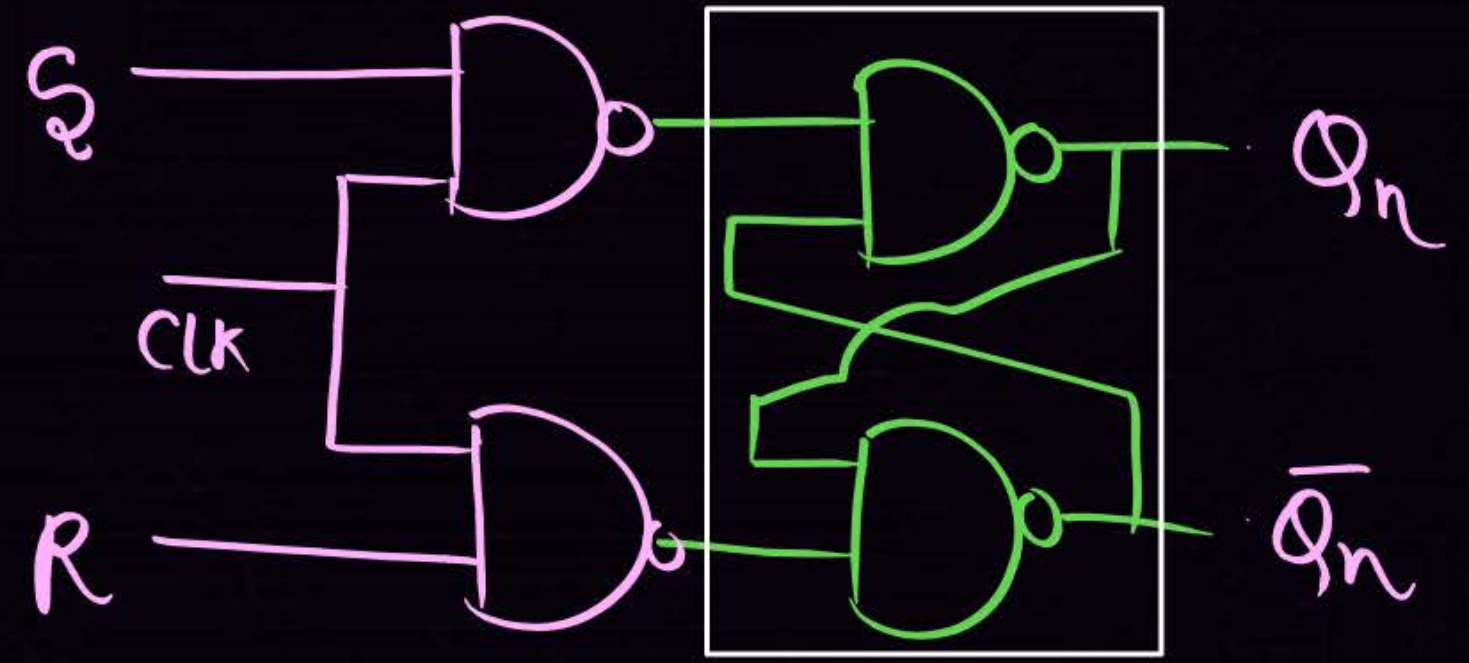

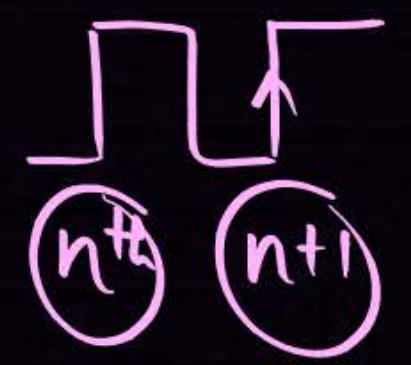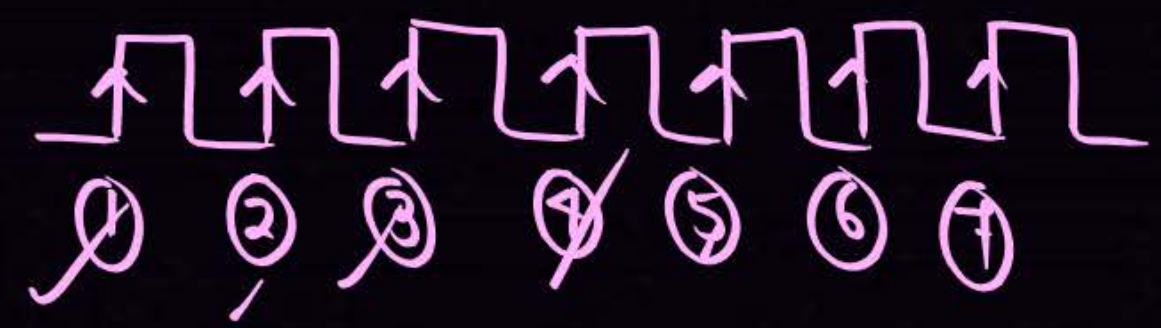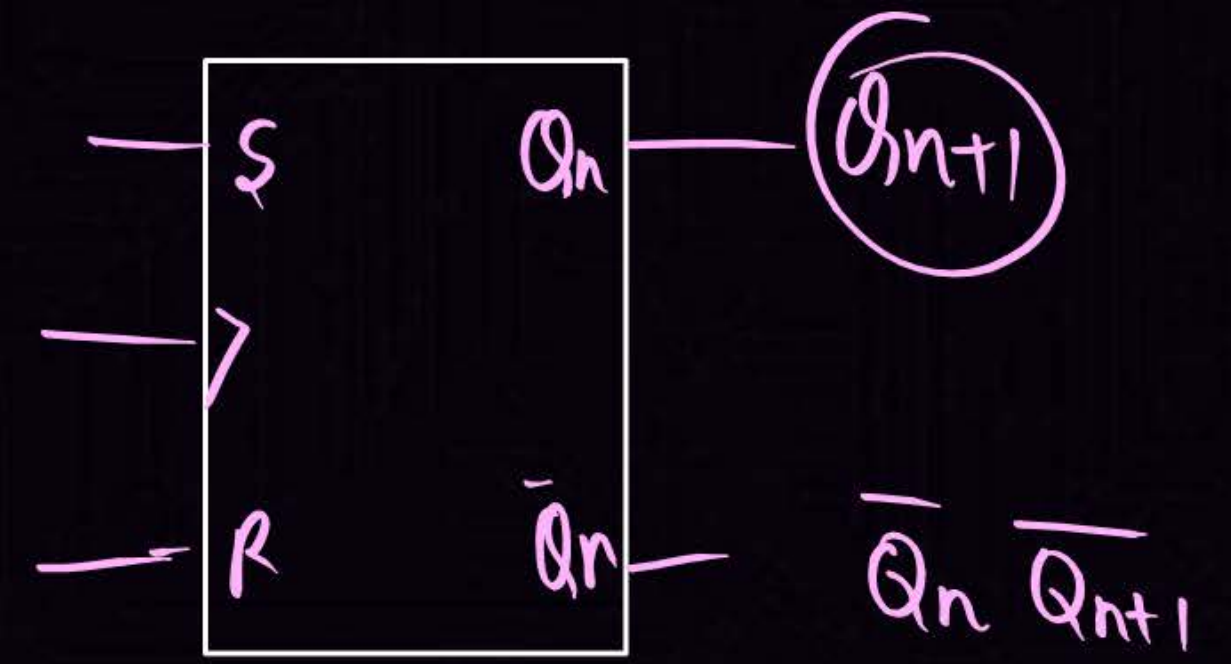
$Q_1 \quad Q_2 \quad Q_3 \quad Q_4 \dots Q_n \quad Q_{n+1}$



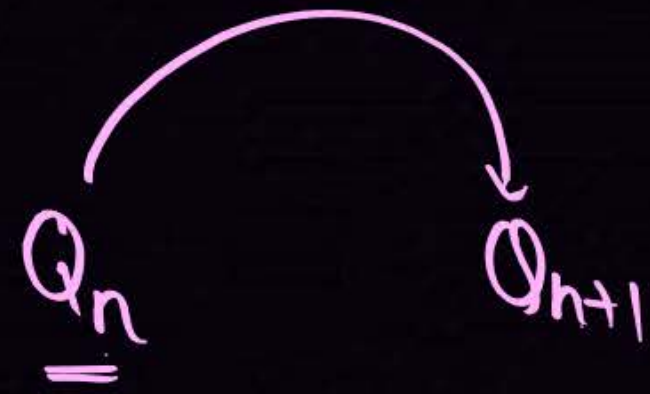


- ① Circuit Diagram / Symbol
- ② Truth Table.
- ③ Characteristic Table.
- ④ Characteristic Equation
- ⑤ Excitation Table.
- ⑥ State Diagram

S	R	F	F
J	K	F	F
H		F	F
T		F	F

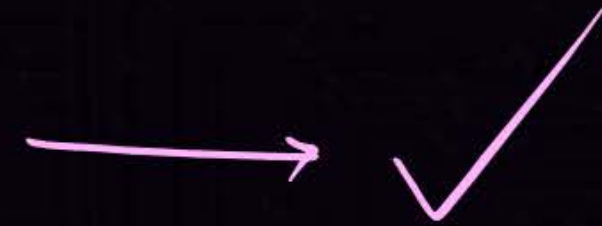

(1) SR FLIP-FLOP [SET RESET FF]

(i) Circuit Diagram :

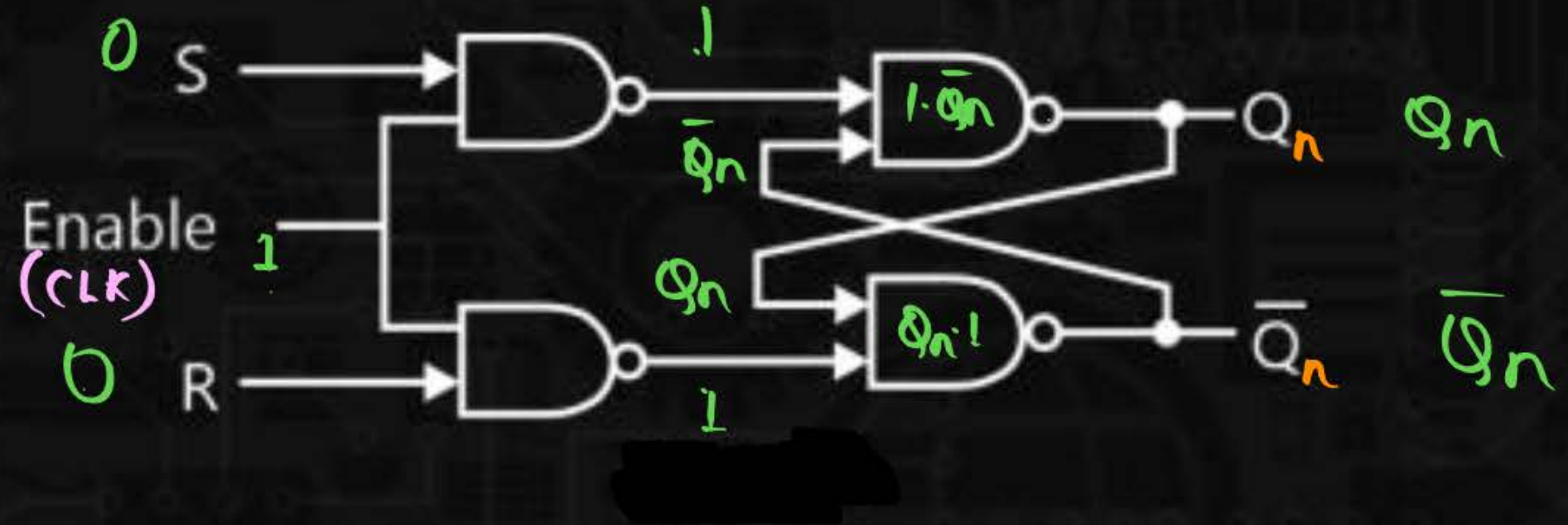

(ii) Truth Table :

S	R	Q_{n+1}	\overline{Q}_{n+1}	
0	0	Q_n	\overline{Q}_n	→ HOLD
0	1	0	1	RESET.
1	0	1	0	SET.
1	1	X	X	Invalid

SR FLIP-FLOP [SET RESET FF]

$$Q_{n+1}(S, R, Q_n) = \sum m(1, 4, 5) + \sum d(6, 7)$$

(iii) Characteristic Table:

	S	R	Q_n	Q_{n+1}
0 →	0	0	0	0
1 →	0	0	1	1
2 →	0	1	0	0
3 →	0	1	1	0
4 →	1	0	0	1
5 →	1	0	1	1
6 →	1	1	0	X
7 →	1	1	1	X

S	R	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	X

$$\left. \begin{matrix} S=0 \\ R=0 \end{matrix} \right\} Q_{n+1} = Q_n$$

$$\left. \begin{matrix} S=0 \\ R=1 \end{matrix} \right\} Q_{n+1} = 0$$

$$\left. \begin{matrix} S=1 \\ R=0 \end{matrix} \right\} Q_{n+1} = 1$$

SR FLIP-FLOP [SET RESET FF]

(iv) Characteristic equations

★


$$Q_{n+1} = S + \bar{R}Q_n$$

		$\bar{R}\bar{Q}_n$ 00	$\bar{R}Q_n$ 01	RQ_n 11	$R\bar{Q}_n$ 10
\bar{S}	0		1		
	S 1	1	1	X	X

SR FLIP-FLOP [SET RESET FF]

(v) Excitation Table


Q_n	Q_{n+1}	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0



S	R	Q_n	Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	X
1	1	1	X

SR FLIP-FLOP [SET RESET FF]







(vi) State Diagram :

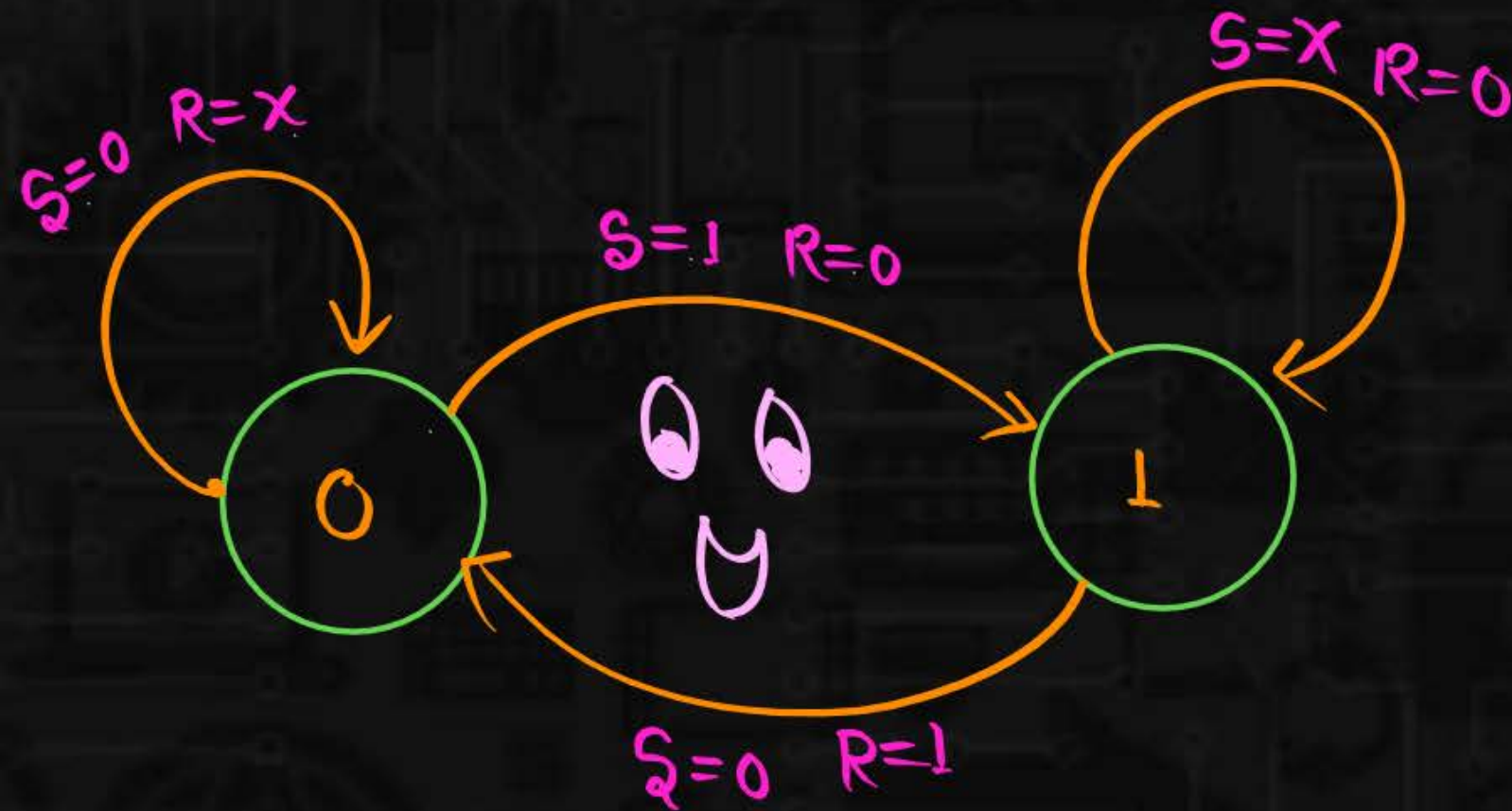

Q_n	Q_{n+1}	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

Q.

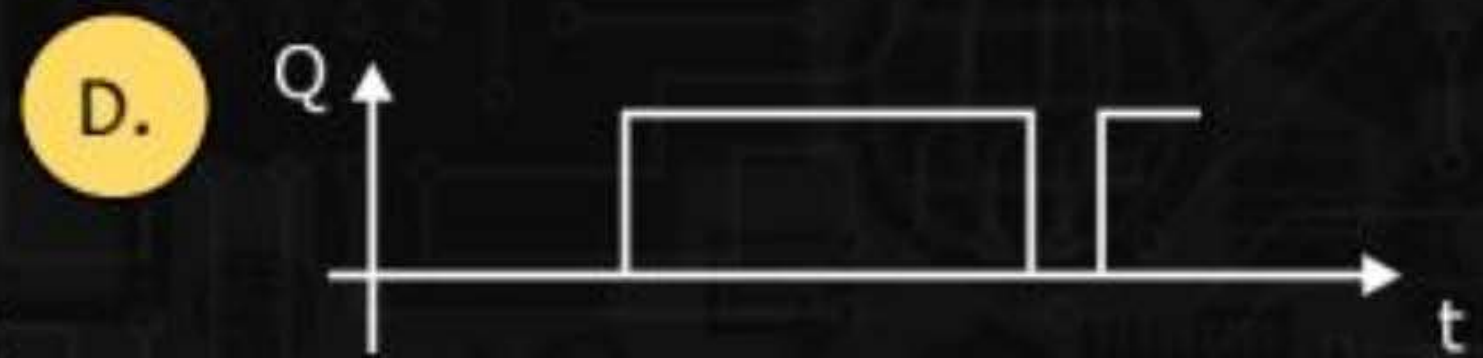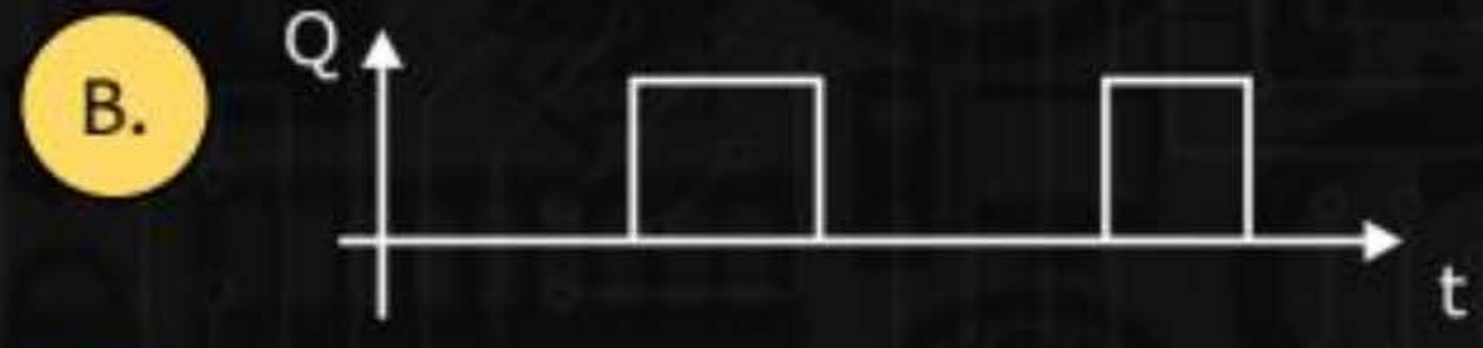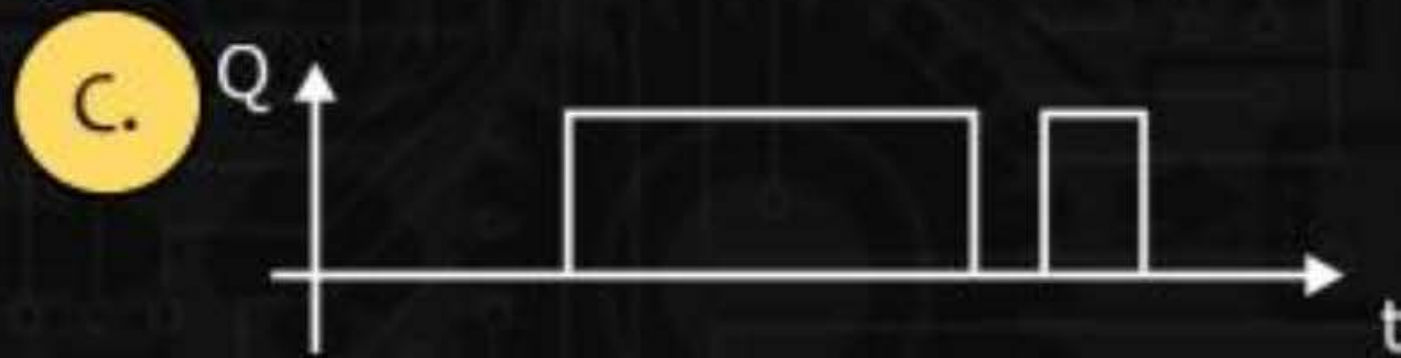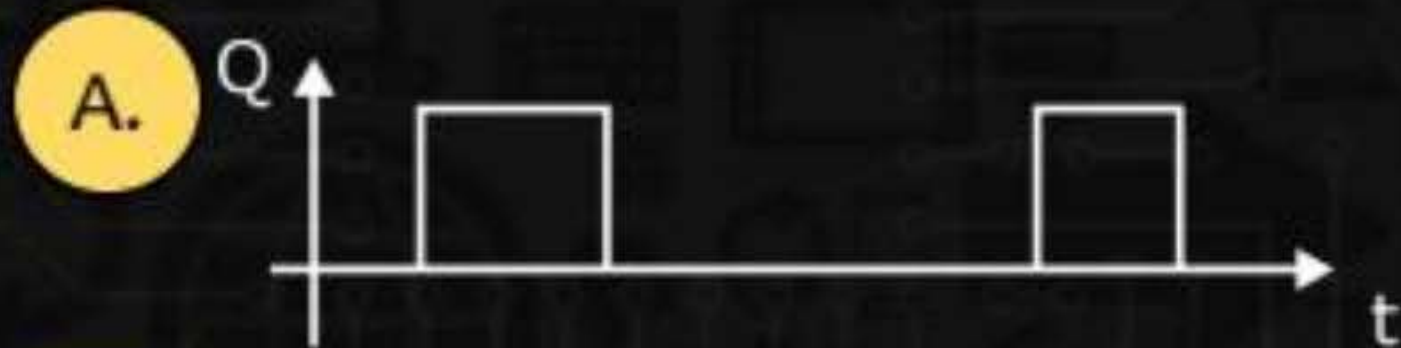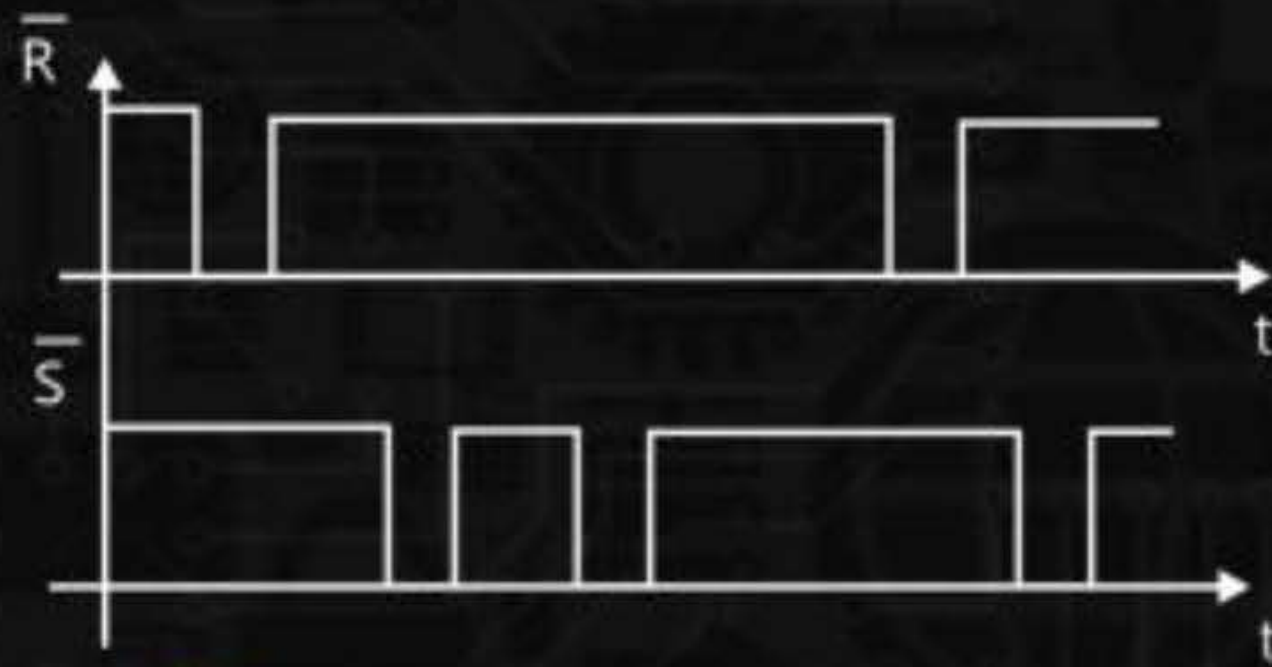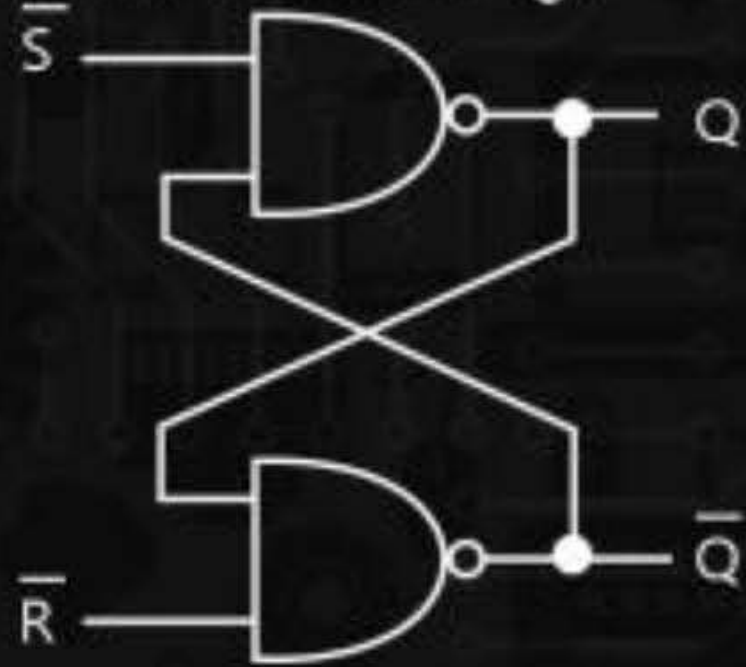The \bar{S} and \bar{R} inputs shown in the figure are applied to a NAND latch. Assuming the Q is 0 initially, which plot gives correct waveform for Q ?



Q. Which of the following will be correct for the given sequential circuit?

A.

The circuit would hold the previous state for $S=0, R=0$

B.


The circuit would hold the previous state for $S=0, R=1$

C.

The circuit would hold the previous state for $S=1, R=1$

D.

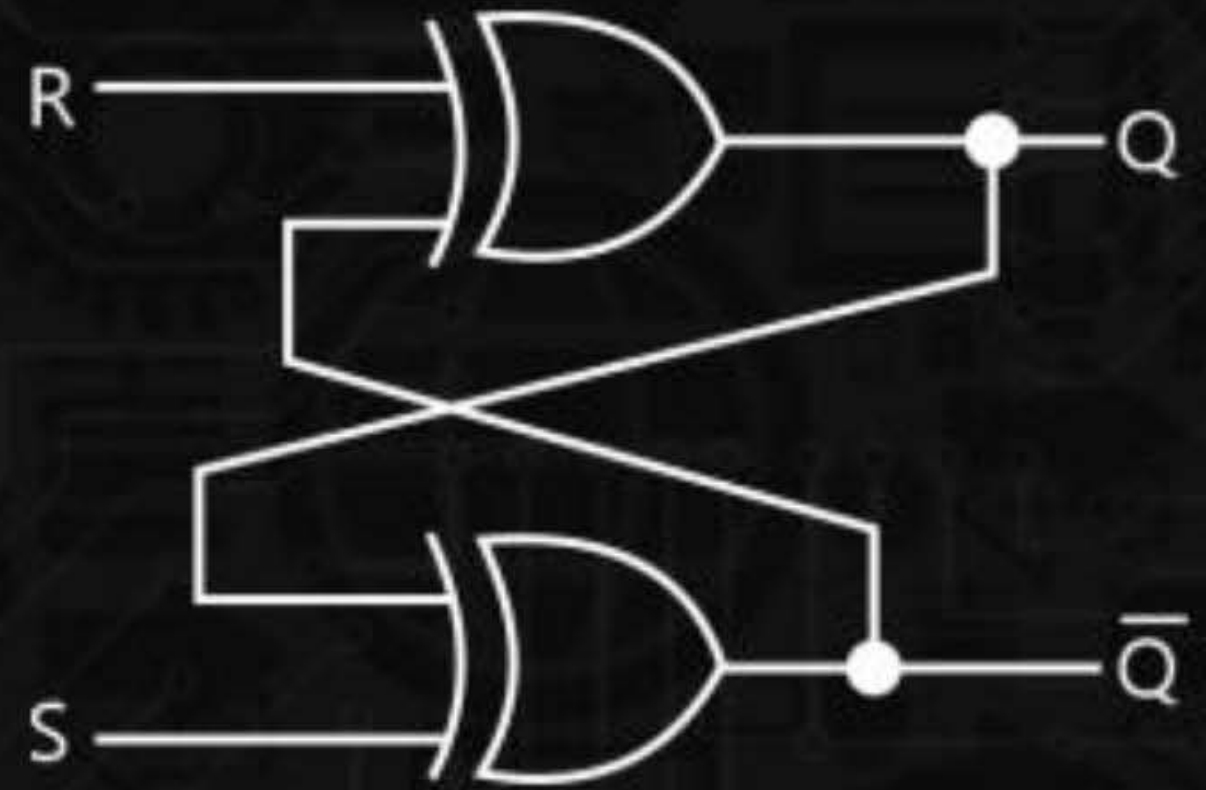The circuit would never be able to hold the previous state under any condition



JK FLIP FLOP

(1) Symbol



Figure 8: JK Flip-Flop

(2) Truth Table

J	K	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	$\bar{Q}_n \rightarrow \text{toggle}$

JK FLIP FLOP



(3) Characteristic Table

J	K	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	\bar{Q}_n

0
①
2
3
④
⑤
⑥
7

J	K	Q_n	Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

JK FLIP FLOP



(4) Characteristic Equation

$$Q_{n+1} = J\bar{Q}_n + \bar{K}Q_n$$

		$J\bar{K}Q_n$ $\bar{K}\bar{Q}_n$ 00	$\bar{K}Q_n$ 01	KQ_n 11	$K\bar{Q}_n$ 10
\bar{J} 0			1		
J 1	1	1			1

JK FLIP FLOP



(5) Excitation Table


Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0



JK FLIP FLOP



(6) State Diagram

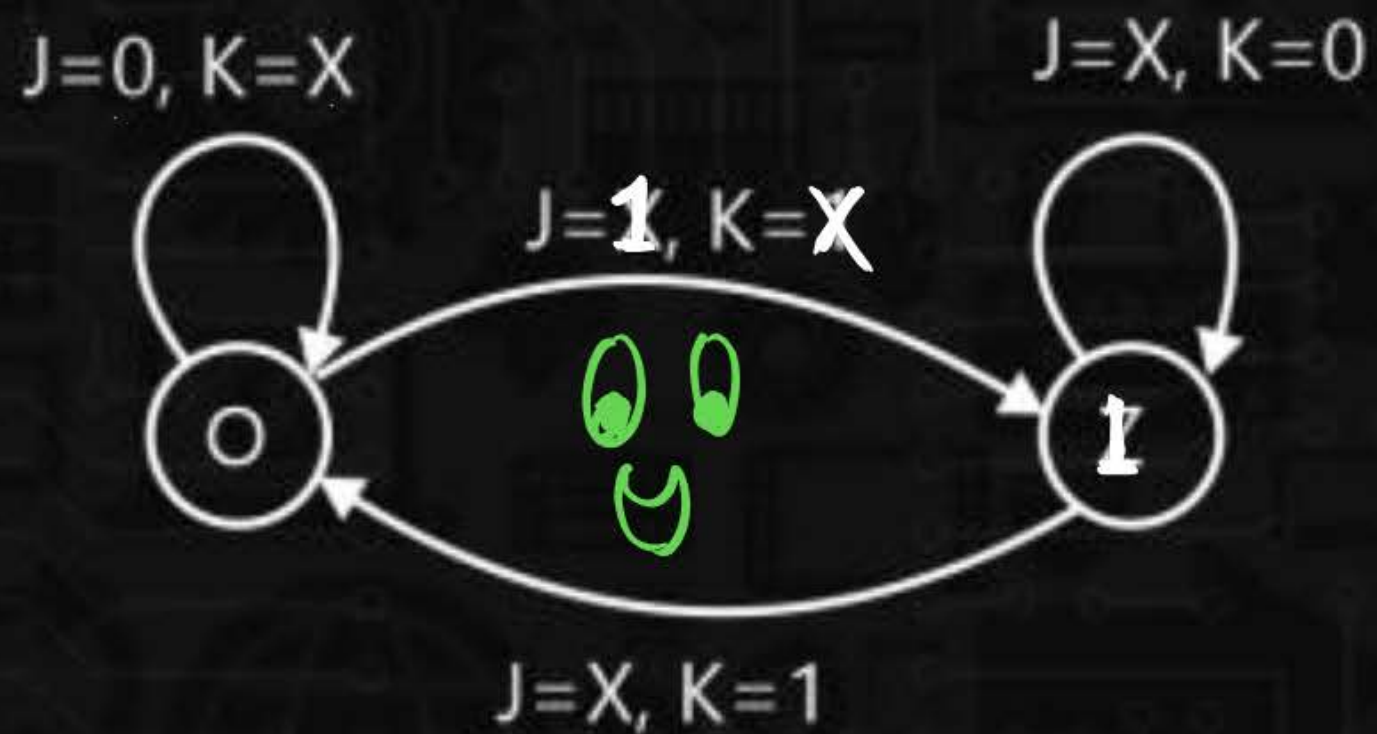

Q_n	Q_{n+1}	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

