

CS & IT ENGINEERING

DIGITAL LOGIC

Combinational Circuit

Lecture No. 6



By- CHANDAN SIR

A stylized illustration of a laptop with an orange base and a blue screen. The screen displays a whiteboard with a blue border containing the text 'TOPICS TO BE COVERED'.

TOPICS TO BE COVERED

A horizontal dotted orange arrow pointing right.

01 MULTIPLEXER

A horizontal dotted orange arrow pointing right.

02 QUESTION PRACTICE

A horizontal dotted orange arrow pointing right.


03 DISCUSSION

A horizontal dotted orange arrow pointing right.


By using 4 x 1 MUX

$$f(A, B, C) = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}\bar{C} + ABC = \sum m(0, 1, 4, 7)$$

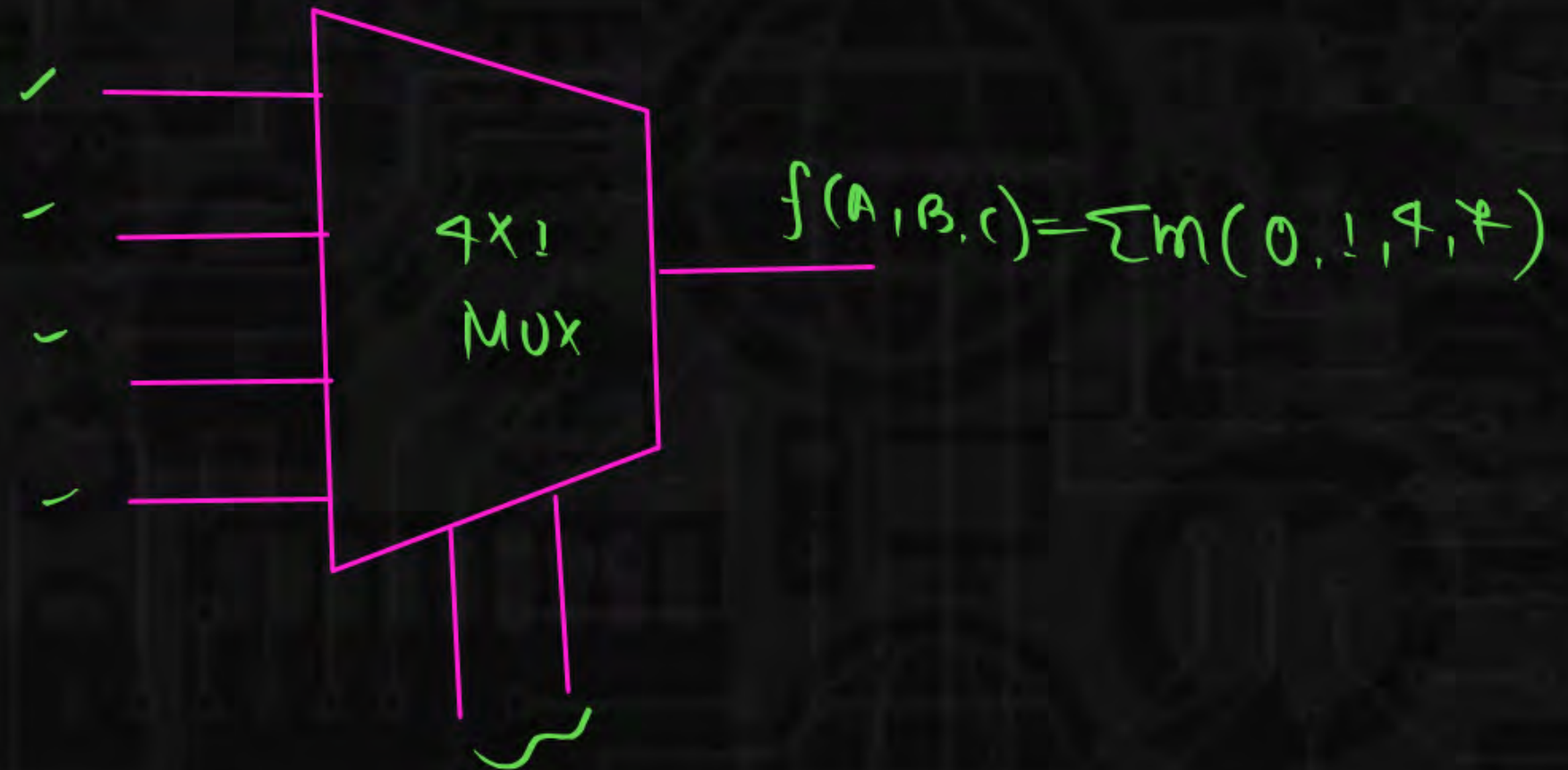- ✓ 1. AB as a select line
- ✓ 2. BC as a select line
- ✓ 3. AC as a select line



1. AB is a select line

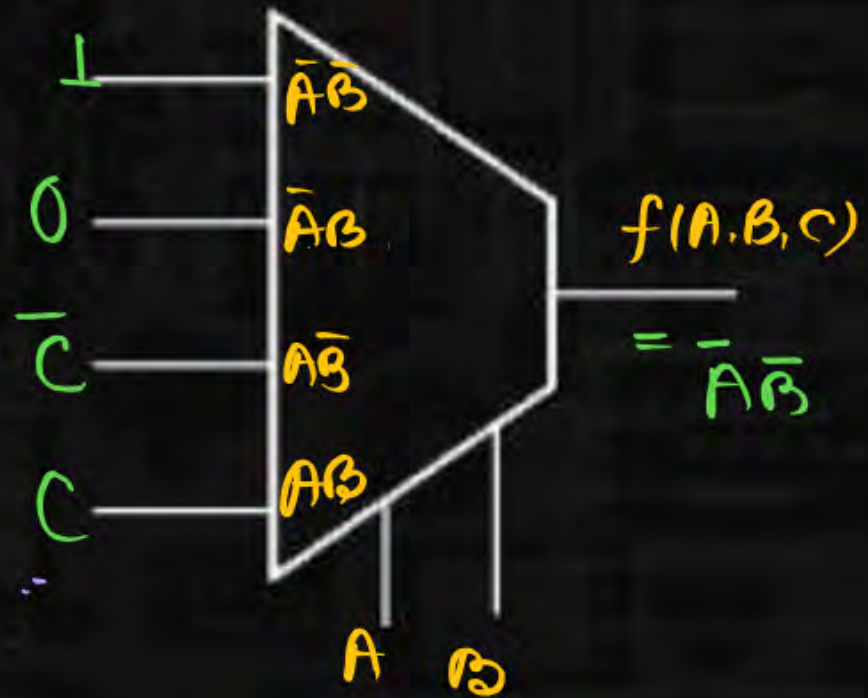


$$f(A, B, C) = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}\bar{C} + ABC$$

$$= \sum m(0, 1, 4, 7)$$

	$\bar{A}\bar{B}$	$\bar{A}B$	$A\bar{B}$	AB
\bar{C}	$\bar{A}\bar{B}\bar{C}$ 0	$\bar{A}B\bar{C}$ 2	$A\bar{B}\bar{C}$ 4	$AB\bar{C}$ 6
C	$\bar{A}B C$ 1	$\bar{A}B C$ 3	$A\bar{B} C$ 5	$AB C$ 7
	1	0	1	0

2. BC is a select line

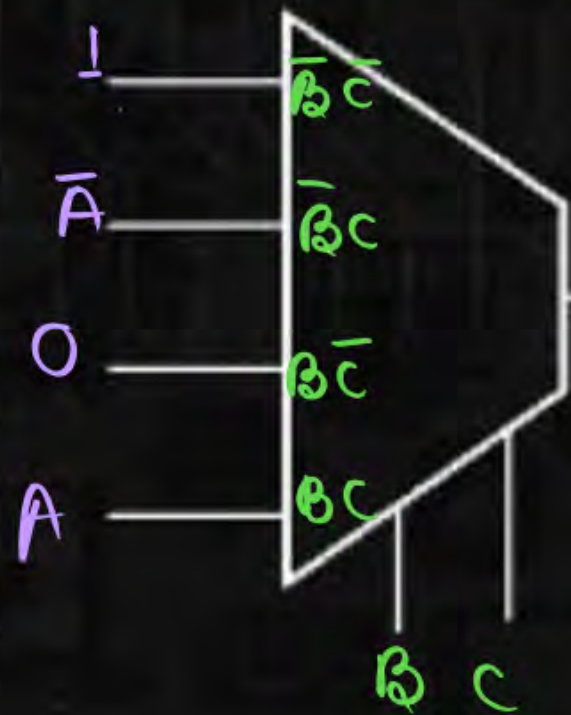


$$\begin{aligned}
 f(A, B, C) &= \bar{B}\bar{C} + \bar{A}\bar{B}C + 0\bar{B}C + AB\bar{C} \\
 &= (\bar{A} + A)\bar{B}\bar{C} + \bar{A}\bar{B}C + AB\bar{C} \\
 &= \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + \bar{A}\bar{B}C + AB\bar{C} \\
 &= \sum m(0, 1, 4, 7)
 \end{aligned}$$

$$\begin{aligned}
 f(A, B, C) &= \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}\bar{C} + ABC \\
 &= \sum m(0, 1, 4, 7)
 \end{aligned}$$

	$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	BC
\bar{A}	$\bar{A}\bar{B}\bar{C}$ 0	$\bar{A}\bar{B}C$ 1	$\bar{A}B\bar{C}$ 2	$\bar{A}BC$ 3
A	$A\bar{B}\bar{C}$ 4	$A\bar{B}C$ 5	$AB\bar{C}$ 6	ABC 7
	1	\bar{A}	0	A

3.

AC as a select line

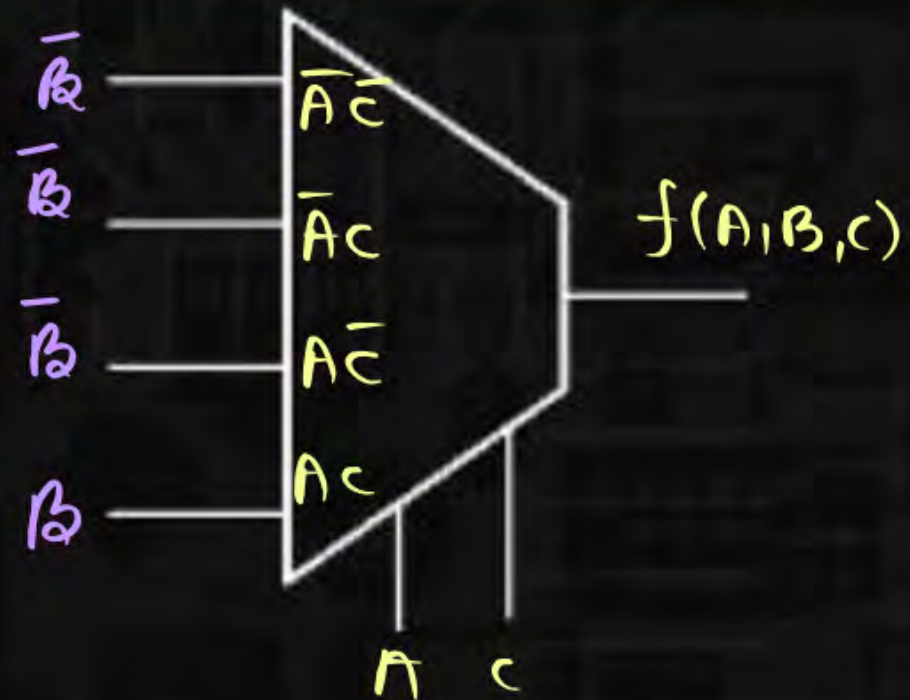


$$f(A, B, C) = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}\bar{C} + ABC$$

$$= \sum m(0, 1, 4, 7)$$

	$\bar{A}\bar{C}$	$\bar{A}C$	$A\bar{C}$	AC
\bar{B}	$\bar{A}\bar{B}\bar{C}$ 0	$\bar{A}\bar{B}C$ 1	$A\bar{B}\bar{C}$ 4	$A\bar{B}C$ 5
B	$\bar{A}B\bar{C}$ 2	$\bar{A}BC$ 3	$AB\bar{C}$ 6	ABC 7
	\bar{B}	\bar{B}	\bar{B}	B

By using 2 x 1 MUX

$$f(A,B,C) = \sum m(0,1,4,7)$$

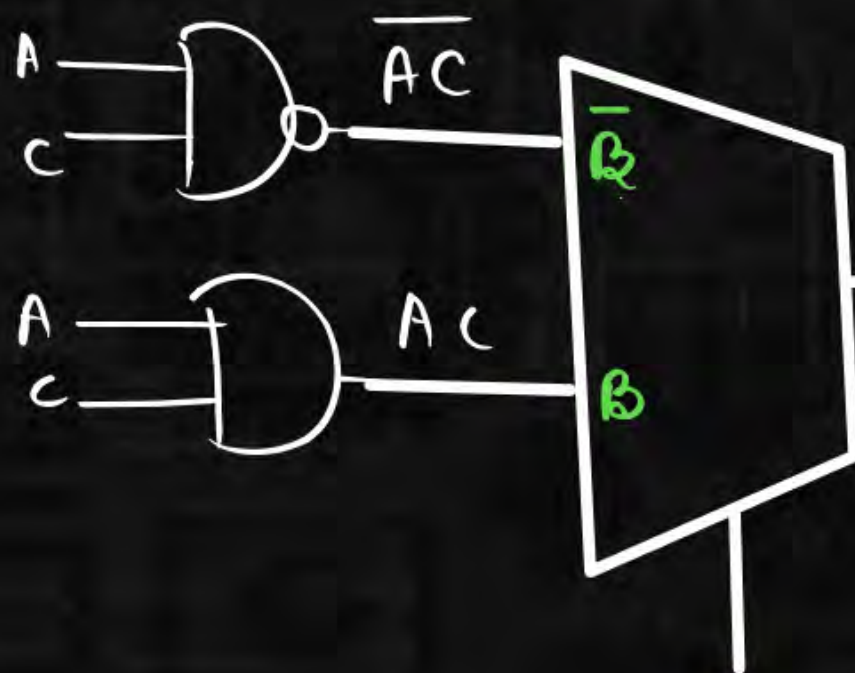

$f(A,B,C)$

$$\bar{A}\bar{C} \cdot \bar{B} + A B C$$

$$(\bar{A} + \bar{C}) \bar{B} + A B C$$

$$\bar{A}\bar{B} + \bar{B}\bar{C} + A B C$$

$$\bar{A}\bar{B}(\bar{C} + C) + (\bar{A} + A)\bar{B}\bar{C} + A B C$$

$$= \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + A B C$$

$$= \sum m(0,1,4,7)$$


$$\bar{A}\bar{C} + \bar{A}C + A\bar{C}$$

$$\bar{A}(\bar{C} + C) + A\bar{C} = \bar{A} + A\bar{C} = \bar{A} + \bar{C} = \overline{A \cdot C}$$

	\bar{B}	B
$\bar{A}\bar{C}$	$\bar{A}\bar{B}\bar{C}$ (0)	$\bar{A}B\bar{C}$ (2)
$\bar{A}C$	$\bar{A}\bar{B}C$ (1)	$\bar{A}BC$ (3)
$A\bar{C}$	$A\bar{B}\bar{C}$ (4)	$AB\bar{C}$ (6)
AC	$A\bar{B}C$ (5)	ABC (7)
$\bar{A} \cdot C$		$A \cdot C$

By using 2 x 1 MUX

$$f(A, B, C) = \sum m(0, 1, 4, 7)$$

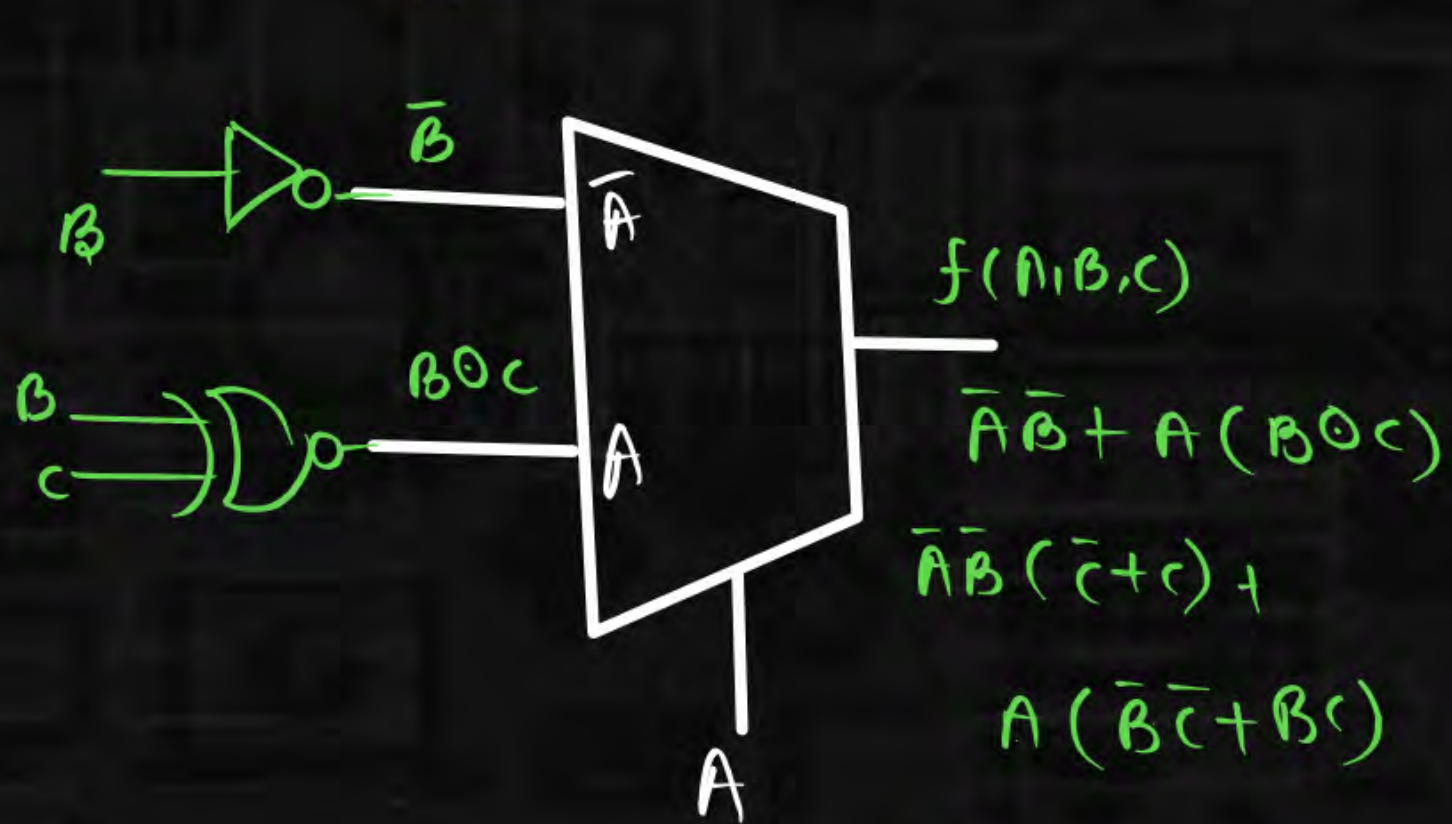

$$\begin{aligned} & \bar{A}\bar{B} + A(B \cup C) \\ & \bar{A}\bar{B}(\bar{C} + C) + \\ & A(\bar{B}\bar{C} + BC) \\ & \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}\bar{C} + ABC \\ & = \sum m(0, 1, 4, 7) \end{aligned}$$

	\bar{A}	A
$\bar{B}\bar{C}$	$\bar{A}\bar{B}\bar{C}$ 0	$A\bar{B}\bar{C}$ 4
$\bar{B}C$	$\bar{A}\bar{B}C$ 1	$A\bar{B}C$ 5
$B\bar{C}$	$\bar{A}B\bar{C}$ 2	$AB\bar{C}$ 6
BC	$\bar{A}BC$ 3	ABC 7
	$\bar{B}\bar{C} + \bar{B}C$ $\bar{B}(\bar{C} + C)$ \bar{B}	$B\bar{C} + BC$ $B \cup C$

Q.

$$f(A, C, B, D) = \sum m(0, 1, 3, 5, 7, 9, 12, 15)$$


- a)
 1. ABD as select line } 8x1 MUX
 2. ACD as a select line. } 8x1 MUX

- b) AB as a select line }
 c) AC as a select line } 4x1 MUX

Type- 6 Delay

$$\begin{cases} T_{AND} = 10 \mu s. \\ T_{XOR} = 15 \mu s. \\ T_{MUX} = 15 \mu s. \end{cases}$$

Ex.

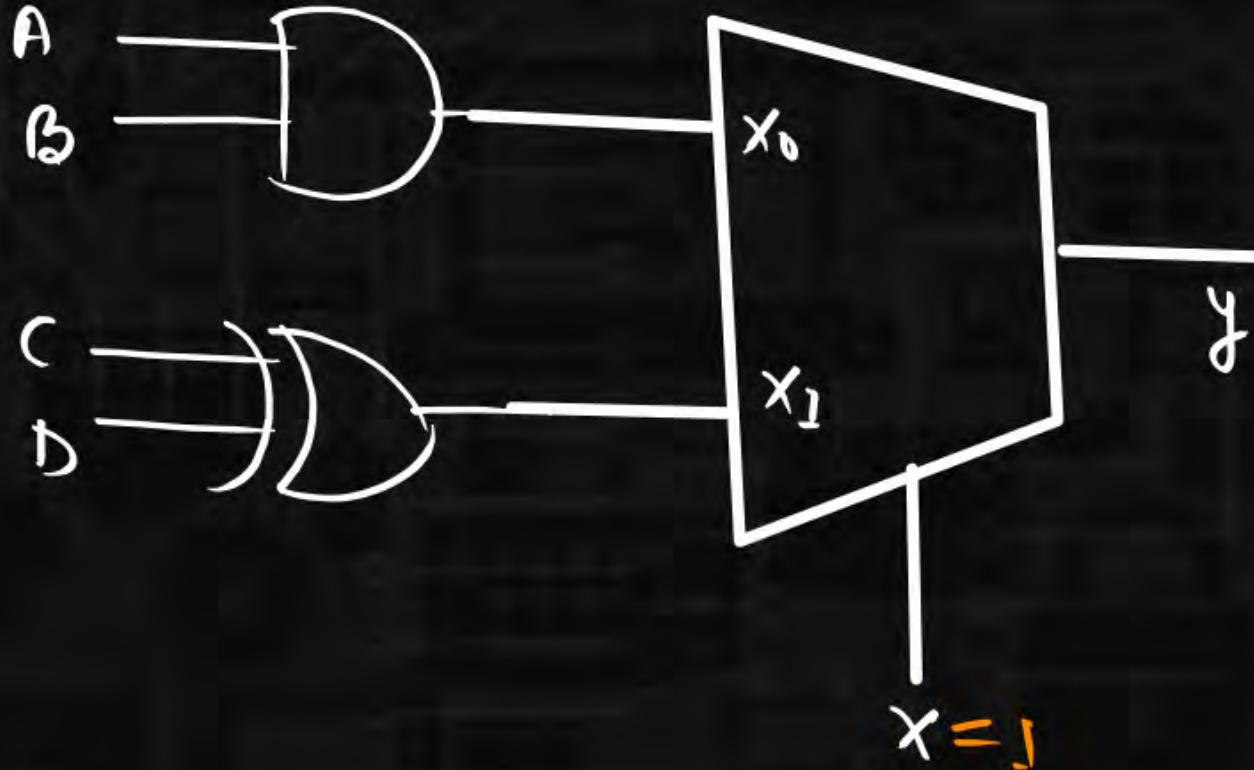

for 'y' find the maximum and minimum Delays?


Case (1) $X = 0$

$$\begin{aligned} T &= T_{AND} + T_{MUX} \\ &= 10 + 15 = 25 \mu s. \end{aligned}$$

Case (2) $X = 1$

$$\begin{aligned} T &= T_{XOR} + T_{MUX} \\ T &= 15 + 15 = 30 \mu s. \end{aligned}$$

Ex.

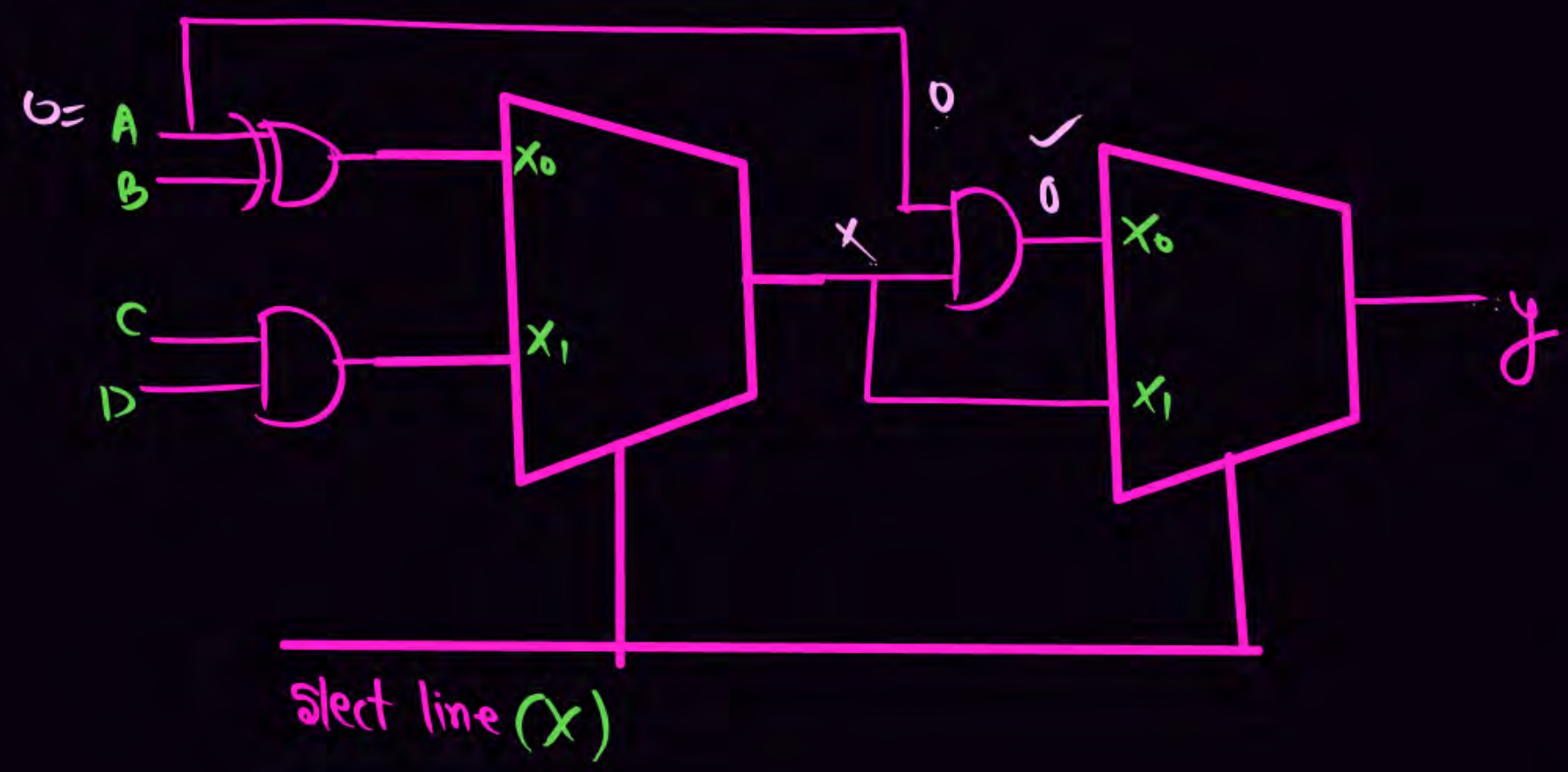

$$T_{XOR} = 2 \mu s$$

$$T_{AND} = 1 \mu s$$

$$T_{MUX} = 2 \mu s.$$

case (1) $X=0$

$$T = T_{XOR} + T_{MUX} + T_{AND} + T_{MUX}$$

$$T = 2 + 2 + 1 + 2 = 7 \mu s =$$

case (2) $X=1$

$$T = T_{AND} + T_{MUX} + T_{MUX}$$

$$= 1 + 2 + 2 = 5 \mu s$$


Q.

P4Q.

The propagation delays of the XOR gate, AND gate multiplexer (MUX) in the circuit shown in the figure are 4 ns, 2 ns and 1 ns, respectively. 😊

If all the inputs P, Q, R, S and T are applied simultaneously and held constant, the maximum propagation delay of the circuit is

- A. 3ns
- B. 6ns
- C. 5ns
- D. 7ns

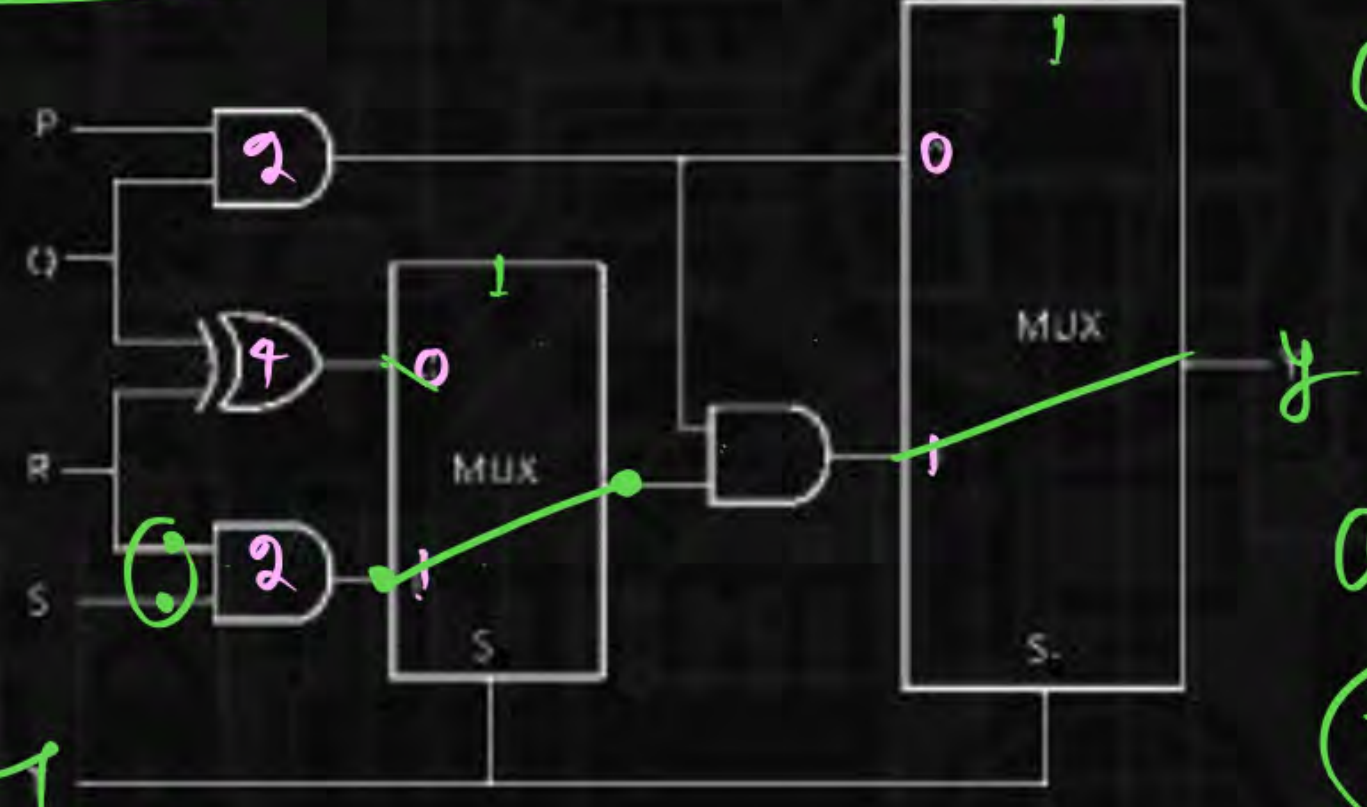

Case (1) $T=0$ 😊
 $T=3\mu s$

Case (2) $T=1$
 $T=6\mu s$

(E) Sir, Mujhe nahi ata,
 kyuki Mai Tare Jameen
 par hu 😊

$T=0$

$\begin{cases} 2 \times 1 \\ 4 \times 1 \\ 8 \times 1 \\ 16 \times 1 \end{cases}$

$\begin{cases} \text{Type(1)} \\ \text{Type(2)} \\ \text{Type(3)} \\ \text{Type(4)} \\ \text{Type(5)} \\ \text{Type(6)} \end{cases}$


HALF Adder कौ बनाने के लिये कितने 2×1 MUX?

$$\text{Sum} = A \oplus B = \bar{A}B + A\bar{B} \longrightarrow \textcircled{2}$$

$$\text{Carry} = AB \longrightarrow \textcircled{1}$$

$$\textcircled{2+1} = \underline{\underline{\textcircled{3}}}$$


D-MUX

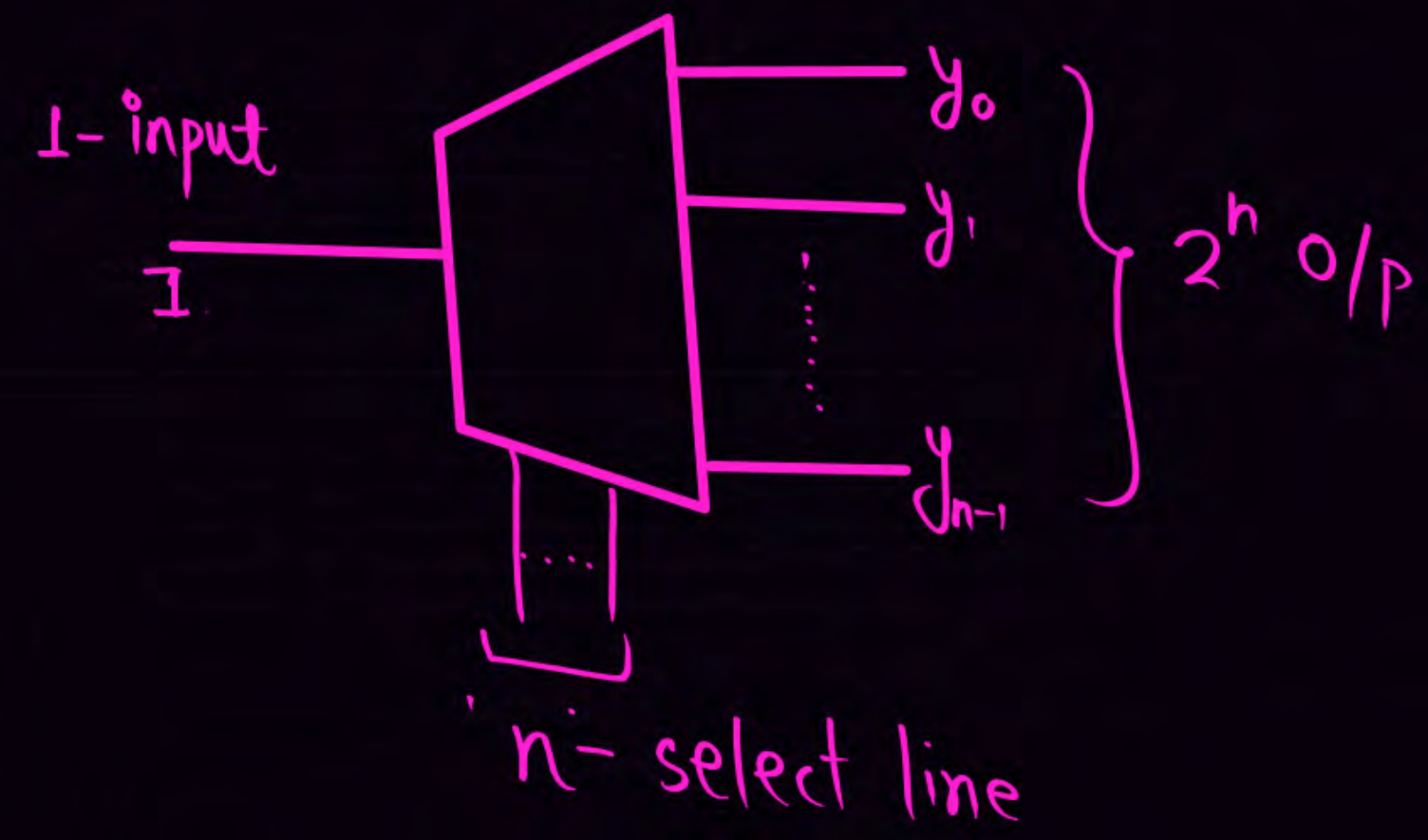

Q.

Design a 1×2 DE-MUX?

Step 1:-

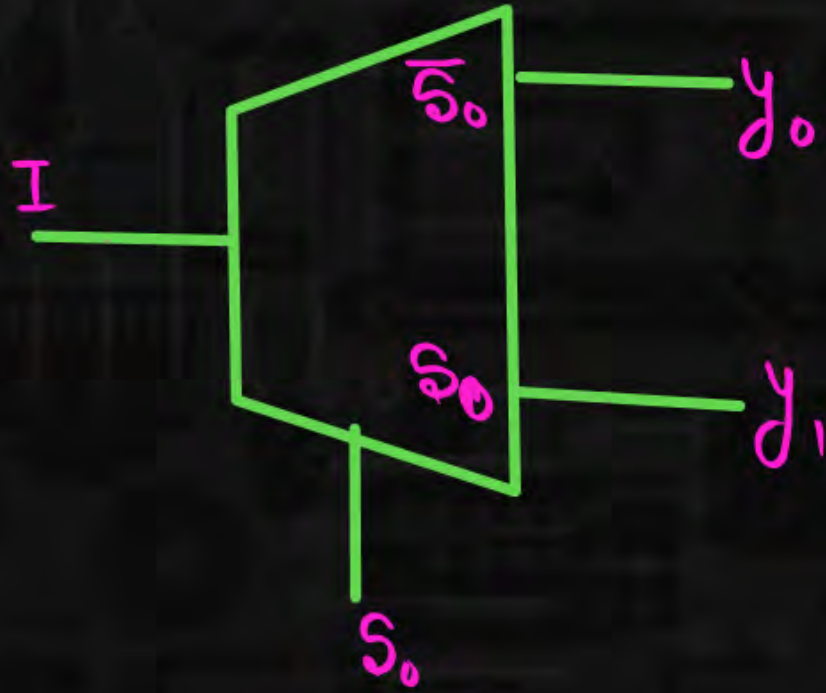

Step 2:


S_0	y_0	y_1
0	I	0
1	0	I

Step 3. $y_0 = \bar{S}_0 I$
 $y_1 = S_0 I$

Step 4: Minimization.

Step 5

$$y_0 = \bar{s}_0 I \quad y_1 = s_0 I$$

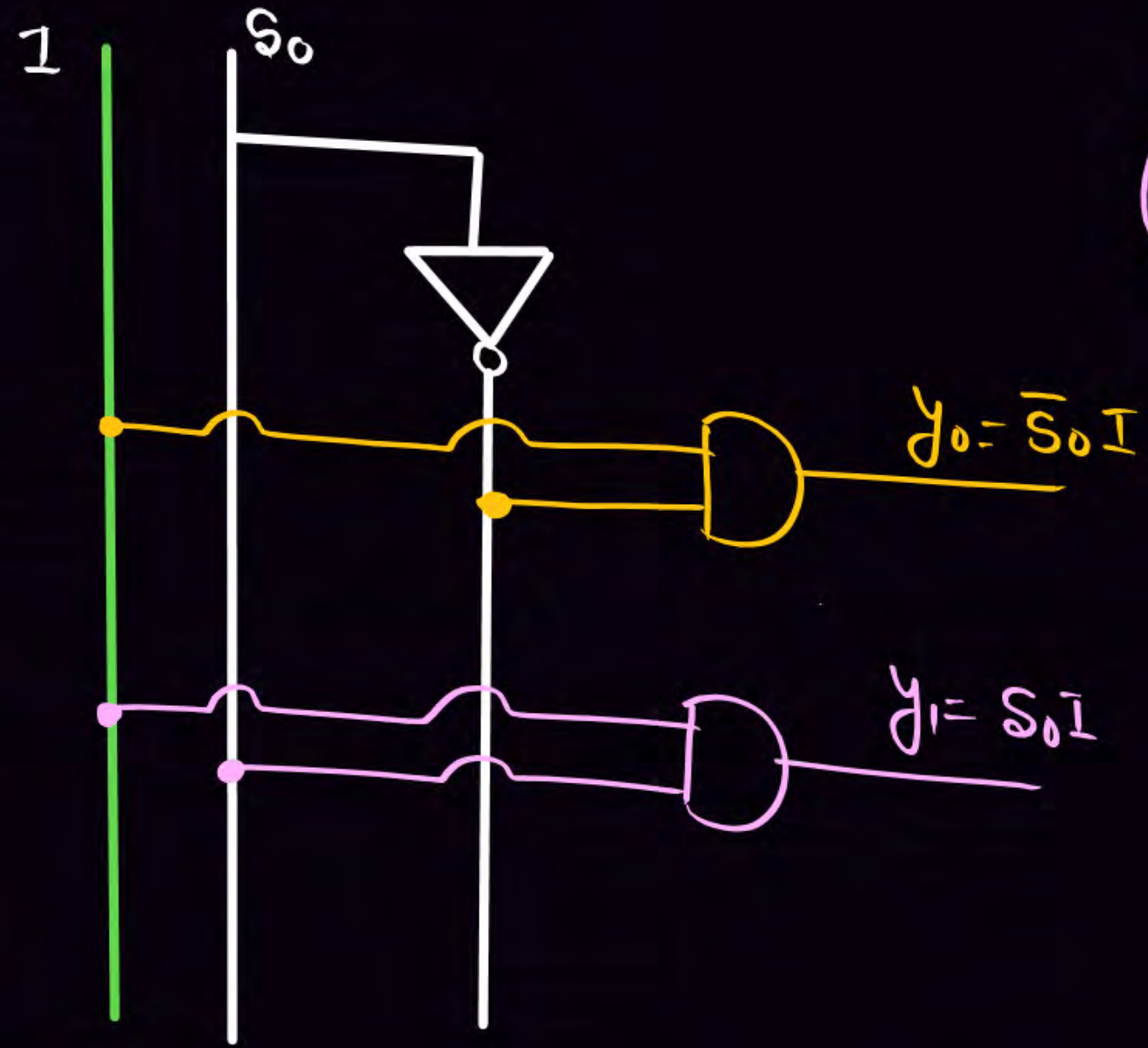


AND Logic

Q.

Design a 1×4 DE-MUX?

Step 1 \rightarrow

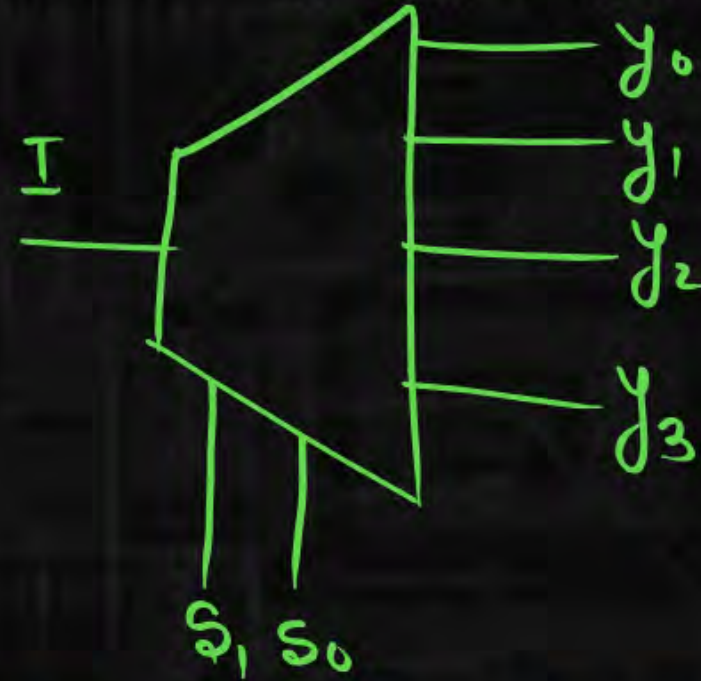

Step 2.

S_1	S_0	Y_0	Y_1	Y_2	Y_3
0	0	I	0	0	0
0	1	0	I	0	0
1	0	0	0	I	0
1	1	0	0	0	I

Step 3. $Y_0 = \bar{S}_1 \bar{S}_0 I$


$Y_1 = \bar{S}_1 S_0 I$

$Y_2 = S_1 \bar{S}_0 I$

$Y_3 = S_1 S_0 I$

Step 4.

Step 5:

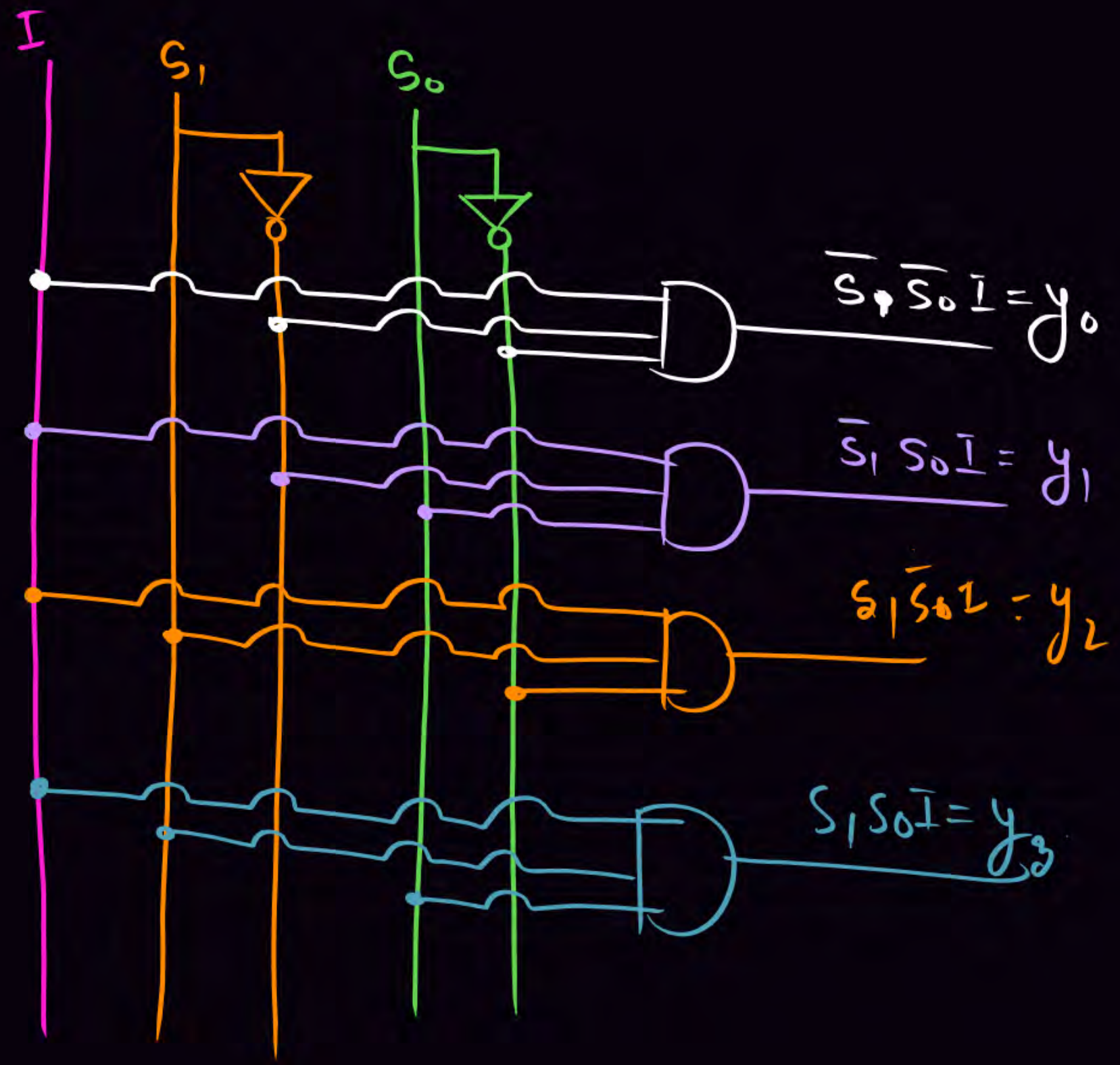

{ 1x8 De-MUX
1x16 De-MUX

H.W

