# CS & IT ENGINEERING



#### DIGITAL LOGIC

(Sequential Circuit)

Latches, SR FF

Lecture No. 1



By- CHANDAN SIR



#### Recape



Basics.

Minimization.

Booleon algebra

(K-MAP)

Combinational circuit


HA, FA, H.S., F.S.

comparator, MUX, DEMUX, Encoder, Decoder, Parallel adder

LA(A)

7 Dolay



 

= 1 final carry


T= (n-1) Tcorry + Max & Tsom, Tcorry

Parallel adder [Ripple corsy adder] AZ BZ A3 B. FA FA FA

#### LOOK AHEAD CARRY ADDER :-





 

#### Citi=GitPici

$$G_1 = A_1 G_1$$


$$S_1 = P_1 \oplus C_1$$


$$f_2 = A_2 \oplus G_2$$

C3= Gy2+ P2 C2

P1= A10 B1

= C42+ P2 G1+ P2 P1 G40+ P2 P1 P0 (0

 

 






Ex.

Y	1 1
+ / .4	- +

 



Seguential circuit


#### SEQUENTIAL CIRCUIT




- A circuit with feedback and memory are called sequential circuit.
- Output of the sequential circuit depends on previous output as well as present state of input.

Mynamic c'icuit



 


Basic memory element

 




Basic memory element

 
- Latches are level triggered
- Latches has two output which is complement of each other




 




$$A = 1 \cdot A$$

 

 



 


X	Y	Q	Q
0	0	L	1 InValid
0	1	7	0
1	0	0	1
1	1	Q	Q → HOLD



A	B	y
0	0	1
0	J	1
1	0	1
۱.	Ţ	Ó

## SR Latch



 


	<u>a</u>	Q	R	S
(1401	ā (	Q	0	0
	1	O	1	0
	0	1	0	1
(in/	T (	1	1	1



 
Note: Whenever S = R = 1 is applied and invalid condition occurs than a NAND having lower propagation delay first change its output and other remain on its previous state are called racing problem or raising problem.






S	R	Q	
0	0		
0	1		
1	0		
1	1		



 


X	Y	Q	
0	0		
0	1	BEEFFE	The same
1	0		
1	1		



 


X	Y	Q	
0	0		
0	1		
1	0	THE PARTY	
1	1	THE BE	



 

X	Y	Q	
0	0		
0	1		
1	0	<b>BUDIES</b>	
1	1	WHEN S	



 


X	Y	Q	
0	0		
0	1		
1	0		
1	1		



Q.1

Consider a latch circuit shown in figure below. Which of the following set of input is invalid for circuit?

 - A. R = 0, H = 0
- B. R = 0, H = 1
- R = 1, H = 1
- D. R = 1, H = 0






Q.2


In the circuit shown below, initially A = 1 and B = 1. The input B is now replaced by a sequence 101010 ..... the outputs X and Y will be

 - A. Fixed at 0 and 1, respectively
- B. Fixed at 1 and 0, respectively
- C. X = 1010..... while Y = 1010....
- D.  $X = 1010 \dots$  while  $Y = 0101 \dots$





(i) Circuit Diagram:

 

(ii) Truth Table:

X	Y	Q	Q
0	0		
0	1		
1	0		
1	1	用外等	



#### (iii) Characteristic Table:

S	R	Qn	$Q_{n+1}$
0	0	0	
0	0	1	
0	1	0	
0	1	1	FIGURE
1	0	0	
1	0	1	
1	1	0	<b>ILEAN</b>
1	1	1	



(iv) Characteristic equations





(v) Excitation Table

Qn	Qn+1	S	R
0	0		
0	1		
1	0		
1	1		

S	R	Q <sub>n</sub>	Q <sub>n+1</sub>
0	0	0	
0	0	1	
0	1	0	
0	1	1	STORY.
1	0	0	
1	0	1	
1	1	0	
1	1	1	


Pw


(vi) State Diagram:


R

Q.

 The S and R inputs shown in the figure are applied to a NAND latch. Assuming the Q is 0 initially, which plot gives correct



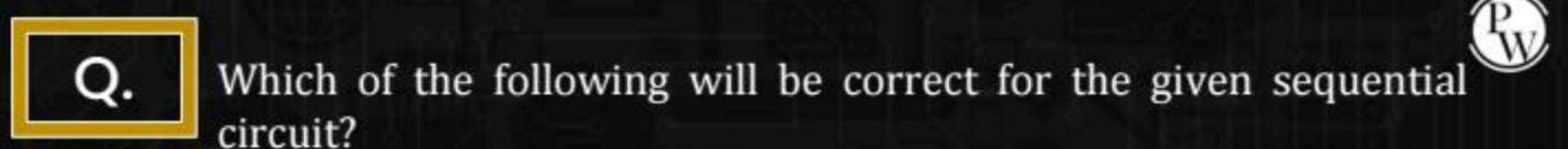


 

The circuit would hold the previous state for S=0, R=1

The circuit would hold the previous state for S=1, R=1

 The circuit would never be able to hold the previous state under any condition





Q.

#### Find the characteristics equation of following excitation table?

A.

$$X Q(t)' + Y' Q(t)$$

В.

$$X + Y'Q(t)$$

C.

$$X Q(t)+Y' Q(t)'$$

D.

$$X+Y'Q(t)'$$

X	Y	Q(t)	Q(t+1)
0	×	0	0
1	0	0	1
0	1	1	0
×	0	1	1

1	0	1
(	W	U
	Ħ	

X	Y	Q <sub>n</sub>	Q <sub>n+1</sub>
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	Est 1

\					
	100		6000	3 400	
				"Cipe	
				Fi 1	

S	R	Q <sub>n</sub>	Q <sub>n+1</sub>
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	7 6-4

S	R	Q <sub>n+1</sub>	02.00
0	0		
0	1		
1	0		
1	1		

Qn	Q <sub>n+1</sub>	S	R
0	0		
0	1		
1	0	Paul	
1	1	- MARIE	W/Jan





