

CS & IT

AND, OR, NAND, NOR GATE



Logic Gate
Lecture No. 2



By- CHANDAN SIR



TOPICS TO BE COVERED 01 AND, OR GATE

01 NAND GATE

02 NOR GATE

03 Discussion

Guidelines to Attend Live Class



- ✓ Attend the class with positive attitude.
- ✓ Punctuality is necessary.
- ✓ Follow the day-wise study plan.
- ✓ Attempt DPP daily as per the schedule.
- ✓ Hold chat while attending the class. We will allow you to ask and put your questions in the comment box.

$$O \cdot 1 = O$$

$$1.0 = 0$$

$$A = A \cdot L$$

$$A = A \cdot A$$

$$0 \cdot A = 0 \quad A \cdot 0 = 0$$

$$O = A \cdot A$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$A+A=A$$

$$A = A + 1 = 1$$


$$A+\overline{A}=1$$

$$A = 0 + A$$

AND GATE

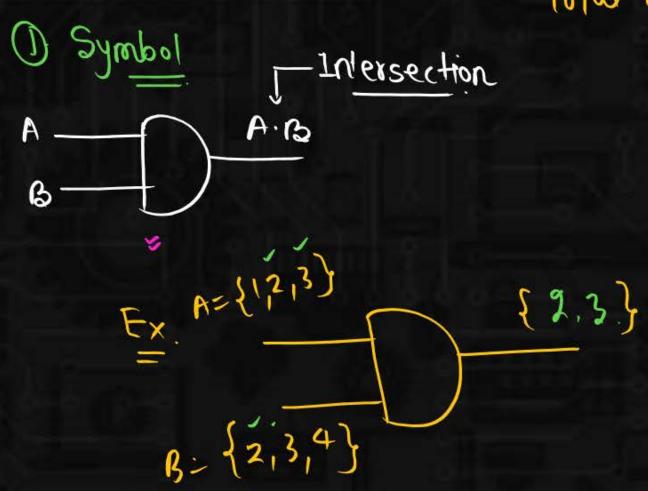"n"-no. of inputs.
Total no. of combination = 2"






2 Truth table.

-> Relation between inpuls & outputs.

A	B	Y=A-B
0	O.	0
0(1	O
1	~ 0	0
L	1	1

AND GATE




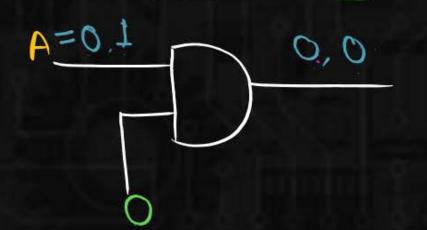

Control o Bisalded

(4) Commutative Law.

$$A \cdot B = B \cdot A$$

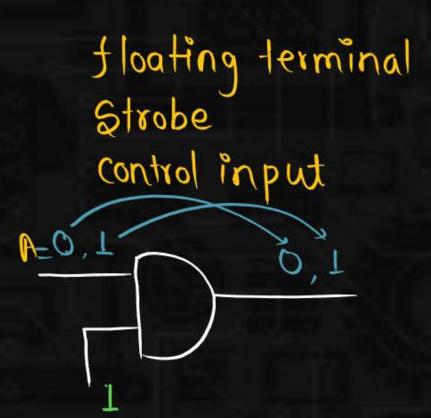

Control '1' Enabled

$$(A \cdot B) \cdot C = A \cdot (B \cdot C)$$



(1) TTL (Transistor - transistor Logic)

Floating terminal always acts as high.

Ex. Logic is designed by TTL, then o/p y will be
The standard of the standa

2) ECL (Emitter coupled Logic)

floating terminal always

acts as a Low


Ex. Logic is designed by ECL, then owput

If loating terminal > 0

A=3.

All services of the services of

OR GATE

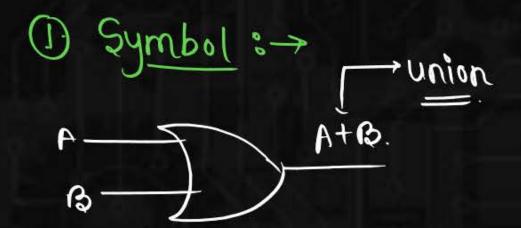

2) Truth Table.

A	B	Y=A+B
0	0	0
0	71	T
1	0	1
1	75	Ţ



3 Enable/Bisable.

$$A=0,1$$
 $O,1$
 $A=0,1$
 $L,1$

Control' O' Enable.

(Ontrol 1' Risabled

(4) Commutative Law.

$$(A+B)+c = A+(B+c)$$

OR GATE



₹5 NOTE

AND, OR

commutative.


Associative



Important Points

- Whenever logic are designed by TTL (Transistor- Transistor logic) then floating terminal always works as a high.
- Whenever logic are designed by ECL (Emitter coupled logic) then floating terminal always works as a low.

MCG

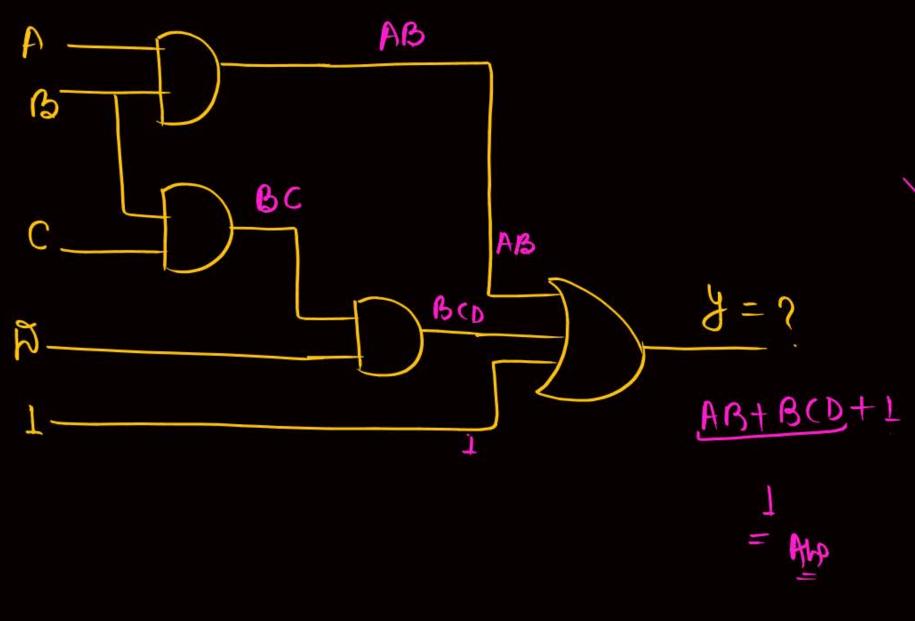

- (A) D
- (8) 1
 - (C) AB
 - (0) Sir, Mujhe nahi ata hai, Mai Tare jameen par hu

If the olp is high then input will be-0= MSQ AB ABC 13 ABC+C = C [AB+1] \times (V) 000 (B)(E) = C. T (B) 00 L \times (c) 010

B-Morgans Law.

$$\frac{\overline{AB}}{\overline{A+B}} = \overline{A+B}$$

$$\overline{A+B} = \overline{A+B}$$

Pw


NAND, NOR GATE

NAND GATE

1) Symbol



2) Truth Table

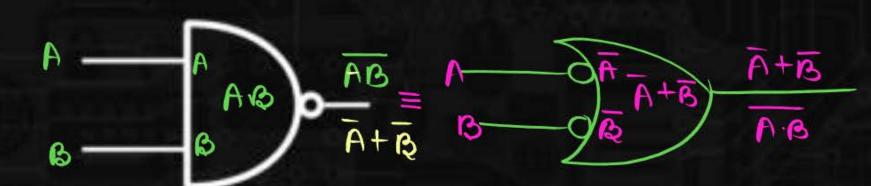


Bubbled OR = NAND






NAND GATE

3) Enable/Disable

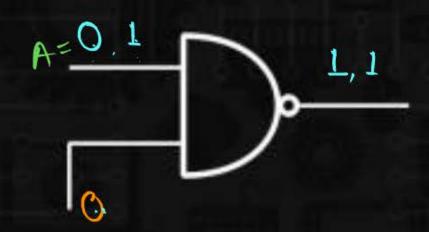

Control o' Disabled

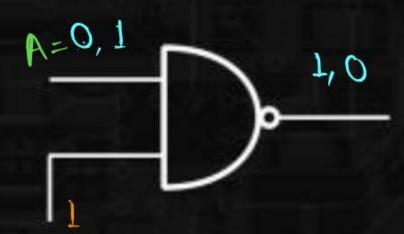


Control, 7, Evapleg



NAND GATE

4) Commutative Law

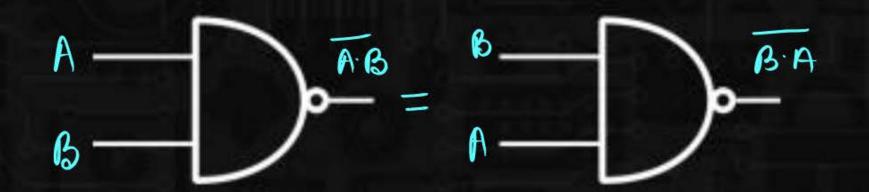

Associative Law. X

 $(\overline{A \cdot B}) \cdot C = A \cdot (\overline{B \cdot C})$


A Do-


BEDOODO


OR GATE, NAND, NOR GATE



NOR GATE

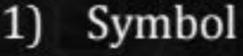


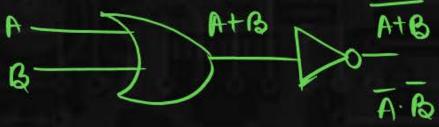

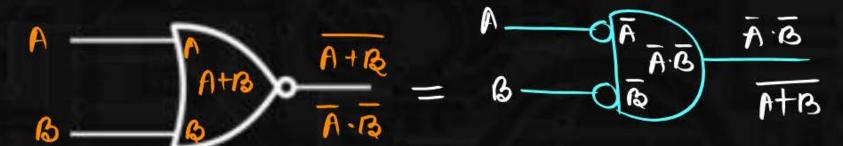

Bubbled AND = NOR


Truth Table

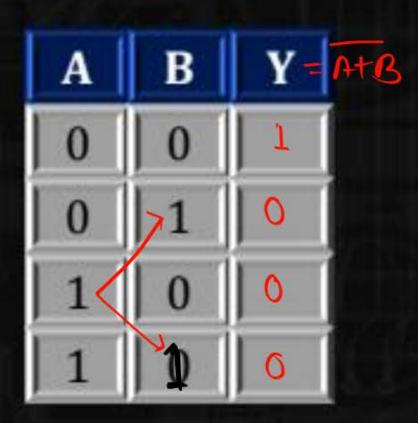




NOR GATE

3) Enable/Disable

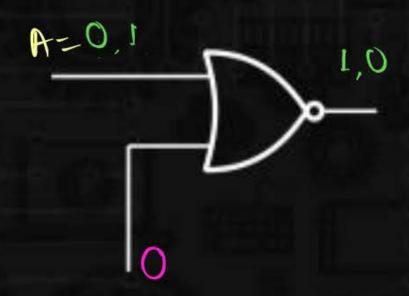

Control o' Enabled

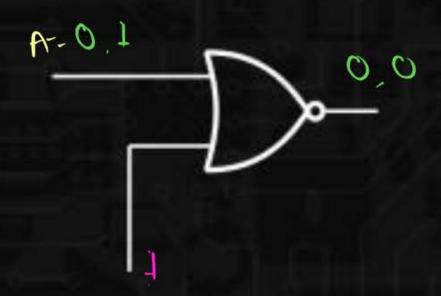

Control 1 Disabled



NOR GATE

4) Commutative Law



Associative Law. Ly does not follow

A
$$A+B$$

(A+B)+c

(A+B)-c

A $A+B$

(B+C)

A+B+C

AB+A


AC+B

(B+C)

A+B+C

NOTE

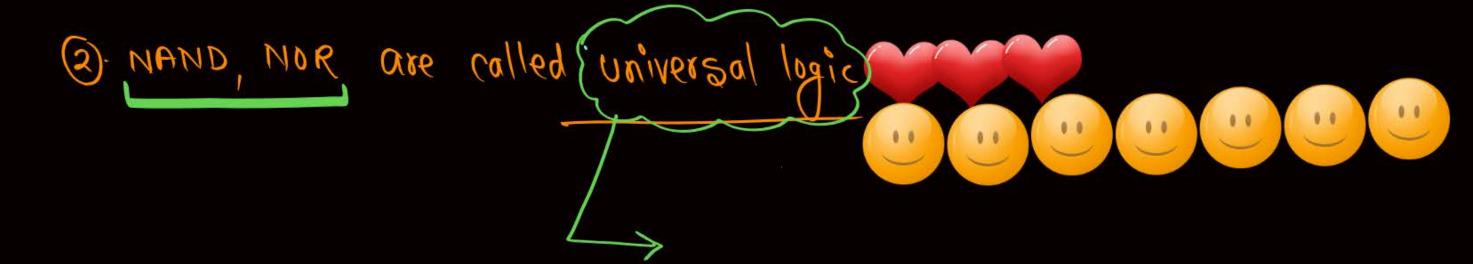1) NAND, NOR follows commutative Law but does not follow associative Law.





Which of the following option universal logic?



(MCQ)

is


- A. NAND
- B. NOR
- Both A & B
- D. None

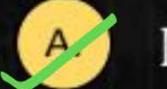Q.2

Which of the following option is called universal logic?







NAND

B. NOR PCTI

Direct coupled Transistor Logic X

c. AND

-> Current Hogging problem

D. OR

Q.3

Which of the following option(s) is/are called universal logic?





$$(A + B)$$


$$(A \cdot B)$$

$$(A \cdot B)$$


$$(A + \overline{B})$$







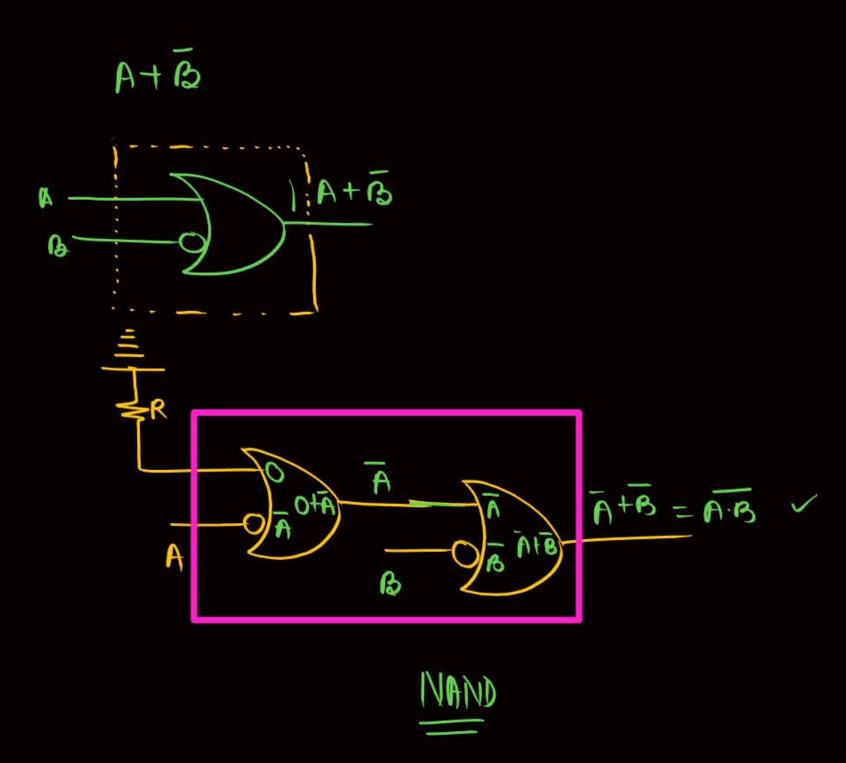

A.B

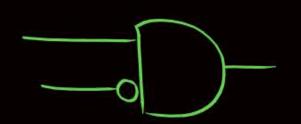

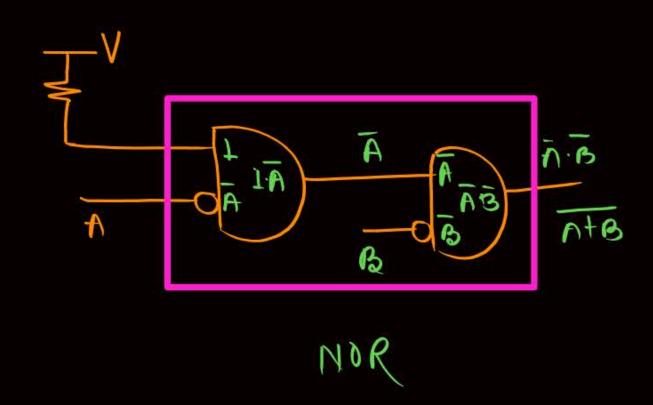

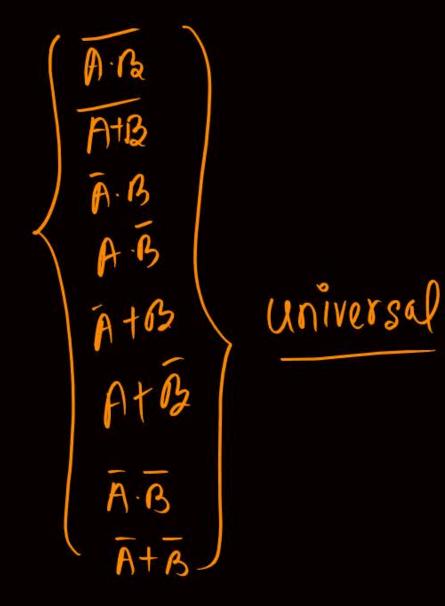




ADE

NAND AS UNIVERSAL LOGIC

- 1) NOT GATE
- 2) AND GATE

4) XOR GATE

5) XNOR GATE

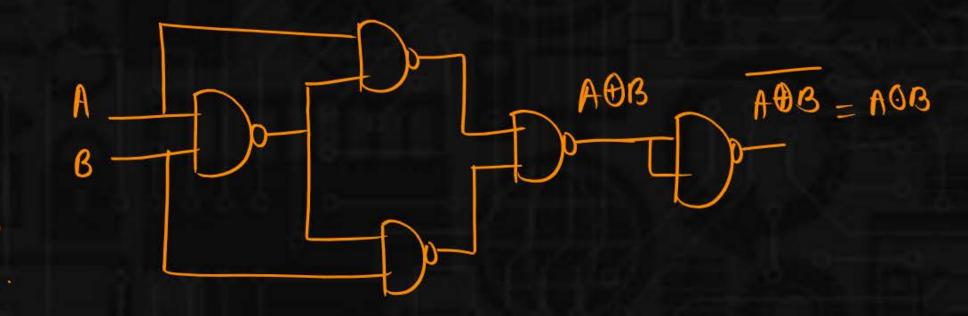

B



Alternate Symbol

Q.4

Find the minimum number of two input NAND GATE required to implement the function- $f(A, B, C) = \overline{A}BC$







